
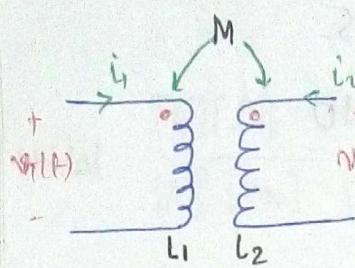


7/11/16

Post 2-Terminal Network (4-Terminals)

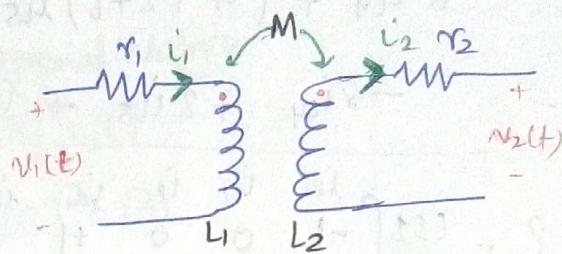

$$W = \frac{1}{2}L_1 i_1^2 + \frac{1}{2}L_2 i_2^2 + M i_1 i_2$$




$$v_1(t) = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$v_2(t) = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$

$$v_1(t) = r_1 i_1 + M \frac{d(-i_2)}{dt} + L_1 \frac{di_1}{dt}$$



$$v_2(t) = r_2 i_2 + L_2 \frac{d(-i_2)}{dt} + M \frac{di_1}{dt}$$

Network f:

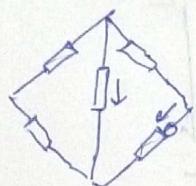

$$H(s) = \frac{\text{I.T. of Response}}{\text{I.T. of Excitation}}$$



1-Port Network

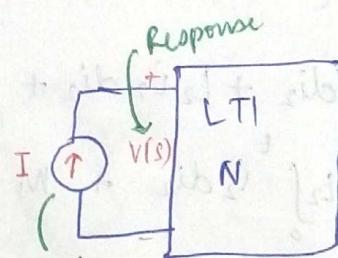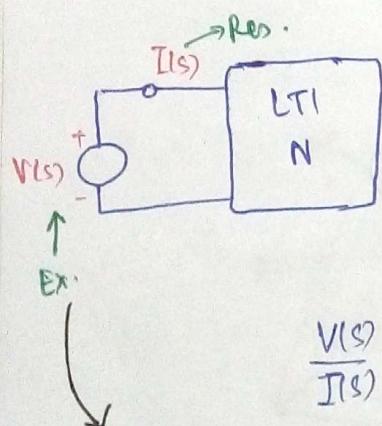



$$\frac{V(s)}{I(s)} = Z(s) = \text{driving point impedance}$$

$$Z(s) Y(s) = 1$$
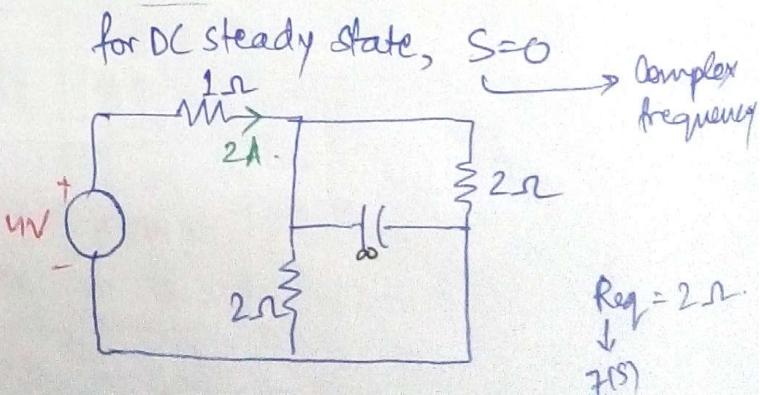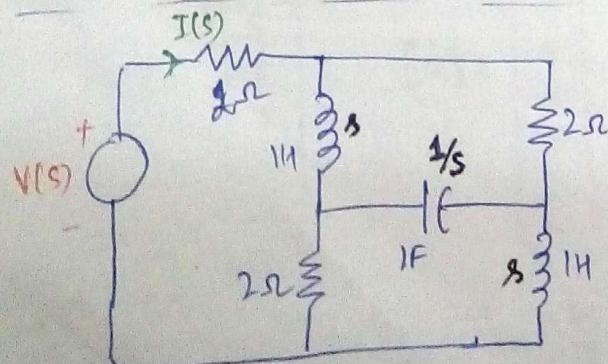
$$\frac{I(s)}{V(s)} = Y(s) = \text{driving point admittance.}$$



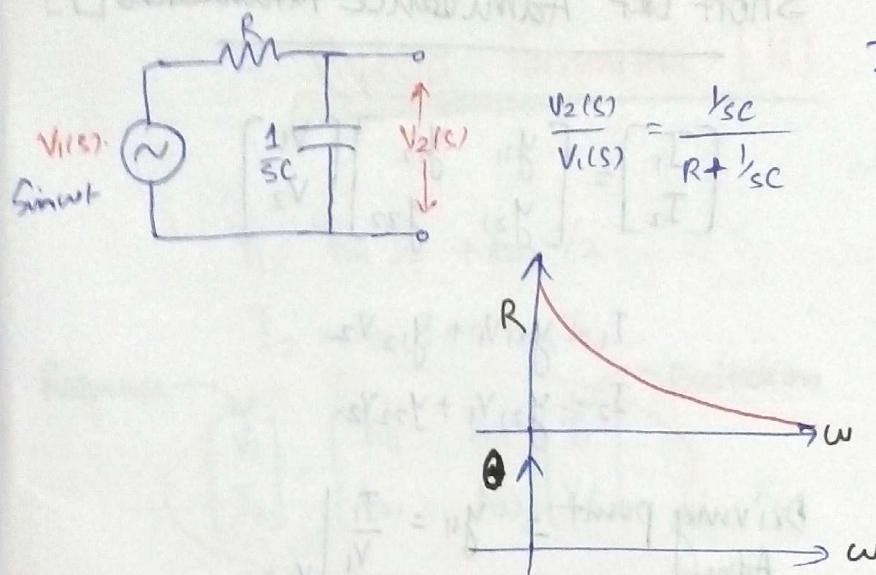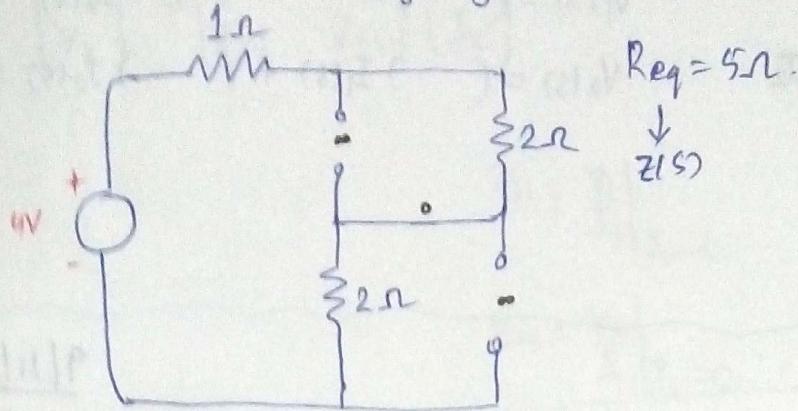
at sinusoid of very high frequency, $s \rightarrow \infty$



If i/p is sinusoidal

$$s = j\omega$$
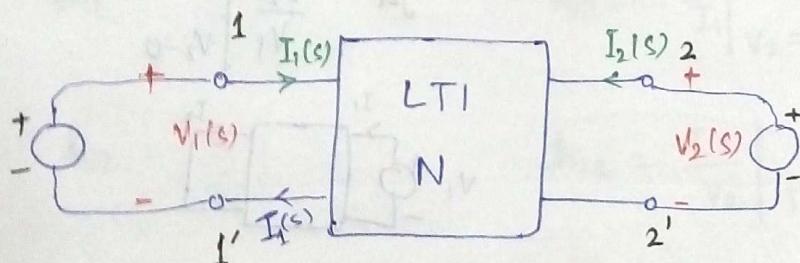
$$\frac{V_2(j\omega)}{V_1(j\omega)} = \frac{\frac{1}{j\omega C}}{R - \frac{1}{j\omega C}} = \frac{\frac{1}{j\omega C}}{\sqrt{R^2 + \frac{1}{\omega^2 C^2}}} \tan(\frac{-1}{\omega C}) = R L \theta.$$



Apply voltages to the port
Responses are $I_1(s)$ & $I_2(s)$

$$I_1(s) = Y_{11} V_1(s) + Y_{12} V_2(s)$$

$$I_2(s) = Y_{21} V_1(s) + Y_{22} V_2(s)$$

$$Y_{11} = \left. \frac{I_1(s)}{V_1(s)} \right|_{V_2(s)=0}$$

$V_2(s) = 0$ (2-2' shorted)


$$Y_{21} = \left. \frac{I_2(s)}{V_1(s)} \right|_{V_2(s)=0}$$

$$Y_{12} = \left. \frac{I_1(s)}{V_2(s)} \right|_{V_1(s)=0}$$

$$Y_{22} = \left. \frac{I_2(s)}{V_2(s)} \right|_{V_1(s)=0}$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Short Ckt. Admittance Matrix

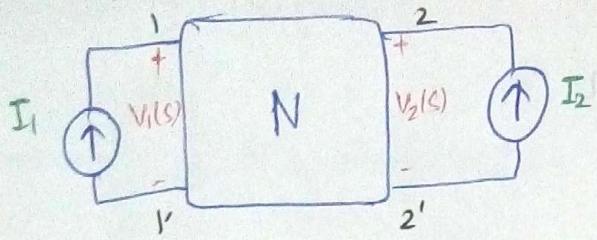


$$V_1(s) = () I_1(s) + () I_2(s)$$

$$V_2(s) = () I_1(s) + () I_2(s)$$

9/11/16

Two Port Network

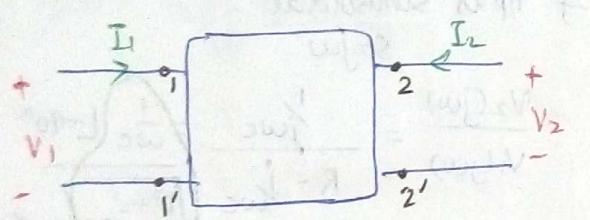

Short ckt Admittance Parameters [Y]

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$


$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

Transfer Admittance
 y_{21} and y_{12}


$$\text{Driving point adm.} = Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}$$

$$Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0}$$

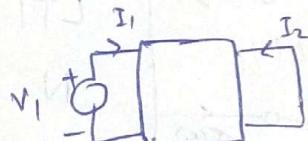


$$Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0}$$

$$Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0}$$

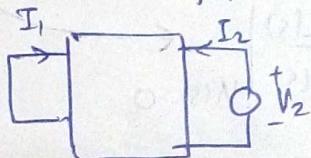

Impedance Matrix

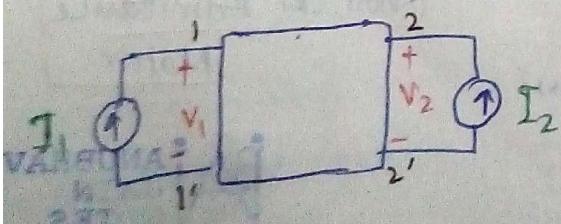


Excitation \rightarrow Current
Voltages \leftarrow Response.

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

Open ckt. - [Z] matrix

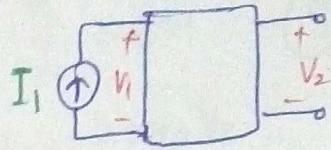

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0}$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$


Hybrid Parameters [H]

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

Response \rightarrow V_1 \rightarrow Excitation I_1
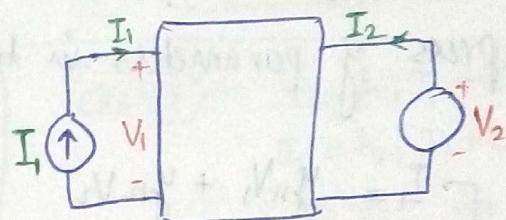
$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$





$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0}$$

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0}$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0}$$

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0}$$

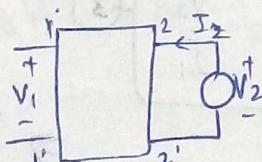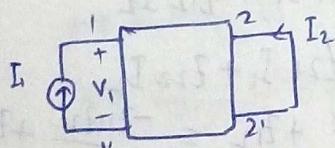


$$\begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ I_2 \end{bmatrix}$$

$$\begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = [H]^{-1} \begin{bmatrix} V_1 \\ I_2 \end{bmatrix}$$

ABCD Parameters
or

Chain parameters

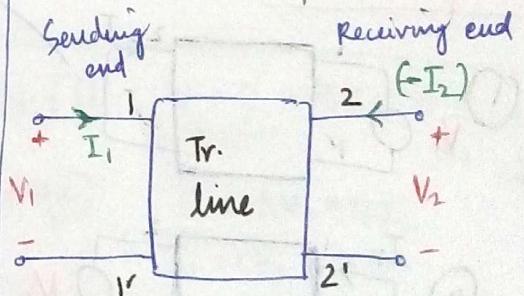

$$V_1 = AV_2 + BI_2$$

$$I_1 = CV_2 + DI_2.$$

$$[T] = \begin{bmatrix} A & B \\ C & D \end{bmatrix}$$

$$A = \frac{V_1}{V_2} \Big|_{I_2=0} \quad ??$$

↓

$$\frac{1}{A} = \frac{V_2}{V_1} \Big|_{I_2=0}$$

$$C = \frac{I_1}{V_2} \Big|_{I_2=0}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

$y \leftrightarrow h$ parameters

Express y parameters in terms of h parameter

$$I_1 = y_{11}V_1 + y_{12}V_2$$



$$I_2 = y_{21}V_1 + y_{22}V_2$$

$$\Rightarrow y_1 = \frac{1}{y_{11}} I_1 - \frac{y_{12}}{y_{11}} V_2 \quad \begin{matrix} \text{compare} \\ \text{coefficients.} \end{matrix}$$

$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$

Reciprocal Networks

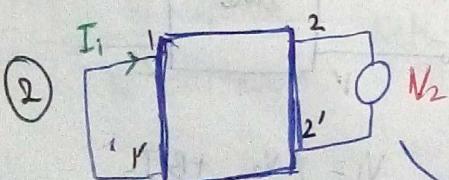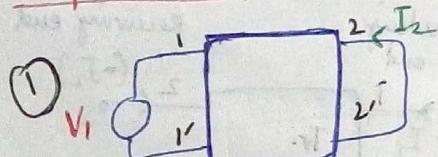

Reciprocity Thm: -

$$\frac{V_1}{I_2} = \frac{V_2}{I_1}$$

$$\bullet V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$\bullet 0 = Z_{21}I_1 + Z_{22}I_2$$

$$\Rightarrow \frac{V_1}{I_2} = \frac{Z_{11}I_1}{I_2} + Z_{12} = -\frac{Z_{11}Z_{22}}{Z_{21}} + Z_{12} \quad ①$$

$$\bullet 0 = Z_{11}I_1 + Z_{12}I_2$$

$$\bullet V_2 = Z_{21}I_1 + Z_{22}I_2.$$

$$\Rightarrow \frac{V_2}{I_1} = Z_{21} + Z_{22} \frac{I_2}{I_1}$$

$$\frac{V_2}{I_1} = Z_{21} + Z_{22} \left(-\frac{Z_{11}}{Z_{21}} \right) \quad ②$$

from ①, ② and ③

$$-\frac{Z_{11}Z_{22}}{Z_{21}} + Z_{12} = Z_{21} + Z_{22} \left(-\frac{Z_{11}}{Z_{21}} \right) \Rightarrow Z_{12} = Z_{21}$$

Similarly, we get

$$y_{12} = y_{21}$$

$$h_{12} = -h_{21}$$

$$AD - BC = 1$$

Ckt. ①

$$I_1 = y_{11}V_1 + 0$$

$$I_2 = y_{21}V_1 + 0$$

$$\frac{V_1}{I_2} = y_{21} \quad \text{--- (5)}$$

Ckt. ②

$$I_1 = 0 + y_{12}V_2$$

$$I_2 = 0 + y_{22}V_2$$


$$\frac{V_2}{I_1} = y_{12} \quad \text{--- (6)}$$

from eqn ③, ⑤ and ⑥

$$\boxed{y_{21} = y_{12}}$$

If network is symmetrical, that means
Driving point Admittances are same

Symmetrical Reciprocal Network

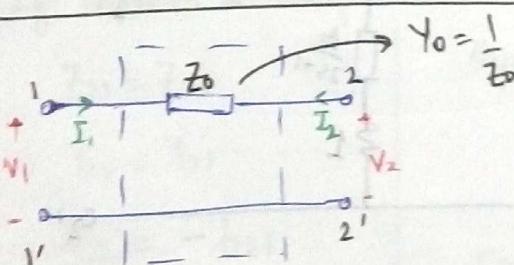

$$\Rightarrow V_1 - I_1 Z_0 = V_2 \quad , \quad I_1 = I_2.$$

$$\Rightarrow I_1 Z_0 = V_1 - V_2$$

$$\Rightarrow I_1 = \frac{1}{Z_0} V_1 - \frac{1}{Z_0} V_2 = Y_0 V_1 - Y_0 V_2 = I_2.$$

$$\Rightarrow I_2 = -Y_0 V_1 + Y_0 V_2.$$

$$\Rightarrow [Z] = [x]$$

$$\Rightarrow [Y] = \begin{bmatrix} Y_0 & -Y_0 \\ -Y_0 & Y_0 \end{bmatrix}$$

$$\text{Ckt. ①} \quad V_1 = h_{11} I_1 + 0$$

$$I_2 = h_{21} I_1 + 0$$

$$\Rightarrow \frac{V_1}{I_2} = \frac{h_{11}}{h_{21}} \quad \text{--- (7)}$$

$$\text{Ckt. ②} \quad 0 = h_{11} I_1 + h_{12} V_2$$

$$\frac{V_2}{I_1} = -\frac{h_{11}}{h_{12}} \quad \text{--- (8)}$$

from eqn ③, ⑦ & ⑧

$$\boxed{h_{21} = -h_{12}}$$

$$\text{Ckt. ①} \quad V_1 = 0 + BI_2 \Rightarrow \frac{V_1}{I_2} = B \quad \text{--- (9)}$$

$$\text{Ckt. ②} \quad 0 = AV_2 + BI_2$$

$$I_1 = CV_2 + DI_2$$


$$C \frac{V_2}{I_1} = 1 - D \frac{I_2}{I_1} = 1 + \frac{DA}{B} \frac{V_2}{I_1}$$

$$\left(C - \frac{DA}{B} \right) \frac{V_2}{I_1} = 1$$

$$\frac{V_2}{I_1} = \frac{B}{BC - DA} \quad \text{--- (10)}$$

from eqn ③, ⑨ and ⑩

$$\boxed{BC - DA = 1}$$

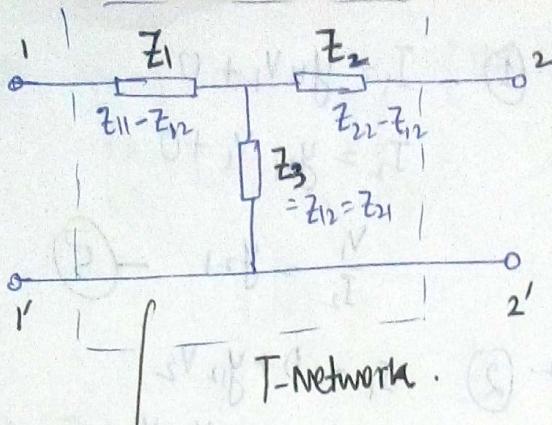

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$


$$* V_1 - I_1 Z_1 - (I_1 + I_2) Z_3 = 0$$

$$\Rightarrow V_1 = (Z_1 + Z_3) I_1 + Z_3 I_2$$





$$* V_2 - I_2 Z_2 - (I_1 + I_2) Z_3 = 0$$

$$\Rightarrow V_2 = I_1 Z_3 + (Z_2 + Z_3) I_2$$
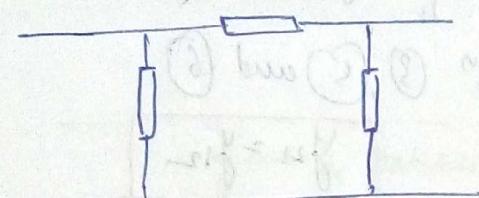
$$[Z] = \begin{bmatrix} Z_1 + Z_3 & Z_3 \\ Z_3 & Z_2 + Z_3 \end{bmatrix}$$




Pi-Network.

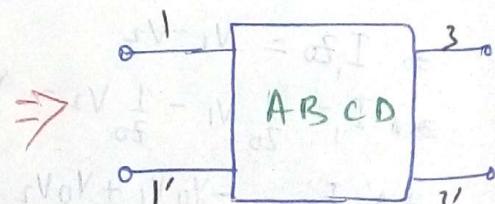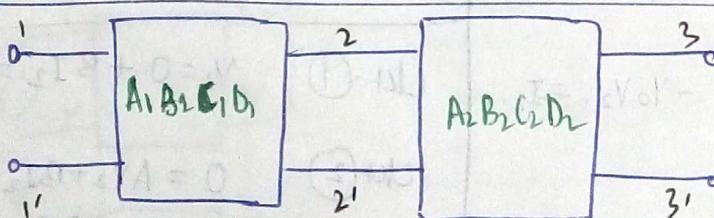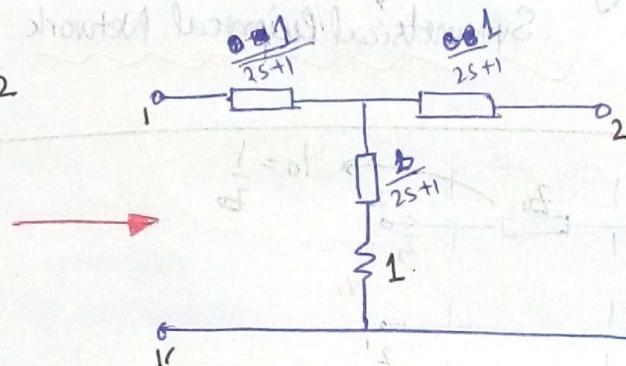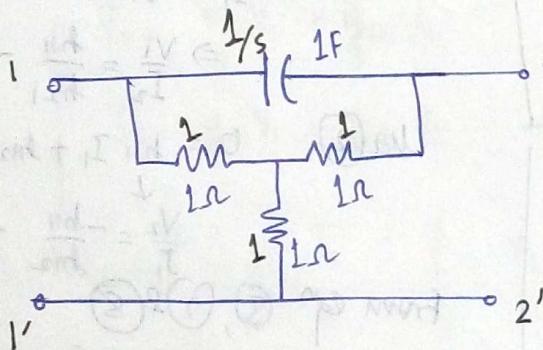

Pass Test - 13/11/16
Date - 11.30 AM
Subject - Cryptograph Theory
Name - Vikram Chilkoor

2-Pot Network

10/11/16

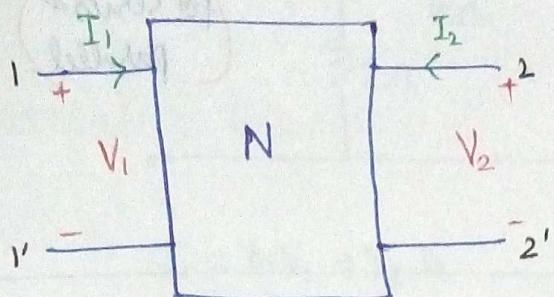

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

$$\begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ I_2 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

If Network is reciprocal :-

$$Z_{12} = Z_{21}$$

$$Y_{12} = Y_{21}$$

$$h_{12} = -h_{21}$$

$$AD - BC = 1$$



Symmetric

$$Z_{11} = Z_{22}$$

$$Y_{11} = Y_{22}$$

$$[T] = ?$$

$$[H] = ?$$

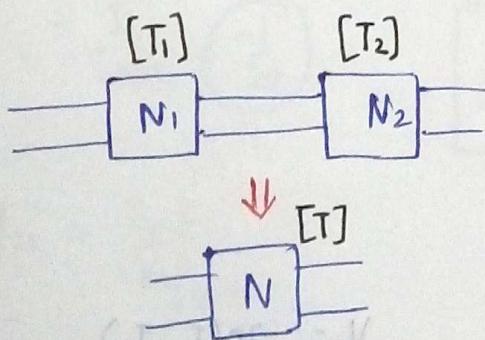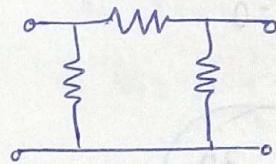


$$[T] = [T_1] \cdot [T_2]$$


(Cascade Networks)

$$[Y] = [Y_1] + [Y_2]$$

(parallel)

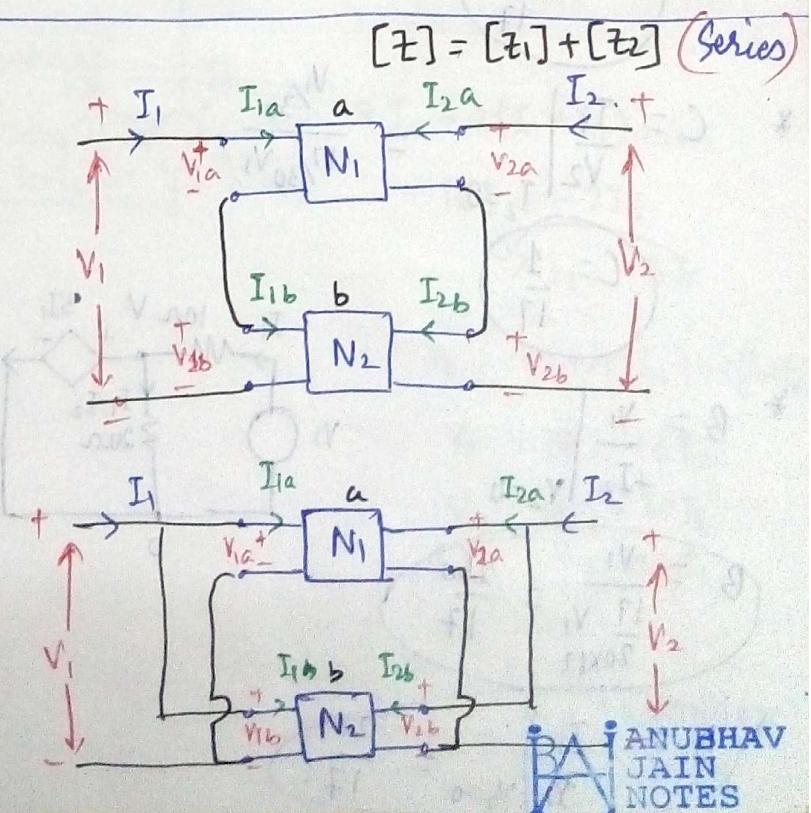


ANUBHAV
JAIN NOTES

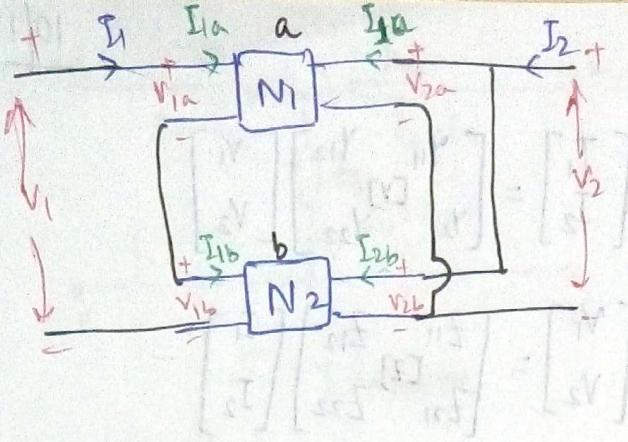

$$[H] = [H_1] + [H_2]$$

(for series & parallel)

Ex.1

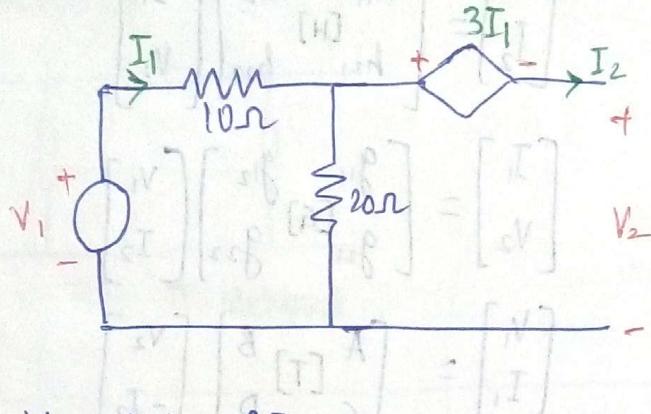

Get A, B, C, D.

$$V_1 = AV_2 + BI_2$$

$$I_1 = CV_2 + DI_2$$

$$* A = \frac{V_1}{V_2} \Big|_{I_2=0}$$

$$\rightarrow V_2 = \frac{20}{30} V_1 - 3(I_1)$$

$$= \frac{2}{3} V_1 - \frac{V_1}{10} = \frac{20-3}{30} V_1 = \frac{17}{30} V_1$$

$$\Rightarrow A = \frac{30}{17}$$


$$* C = \frac{I_1}{V_2} \Big|_{I_2=0} = \frac{V_1/30}{17/30 V_1}$$

$$C = \frac{1}{17}$$

$$* B = \frac{V_1}{V_2} \Big|_{I_2=0} = \frac{V_1}{17 V_1} = \frac{1}{17}$$

$$B = \frac{V_1}{17 V_1} = \frac{20}{17}$$

$$* D = \frac{I_1}{V_2} \Big|_{V_2=0} = \frac{20}{17}$$

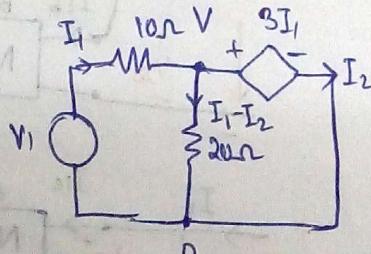

$$V = 20(I_1 - I_2)$$

$$= V_1 - 10 I_1$$


$$= 3I_1$$

$$\Rightarrow V_1 = 13I_1 \Rightarrow I_1 = \frac{V_1}{13}$$

$$17I_1 = 20I_2 \Rightarrow I_2 = \frac{17}{20} I_1$$

$$= \frac{17}{20} \left(\frac{V_1}{13} \right)$$

Ex. 2

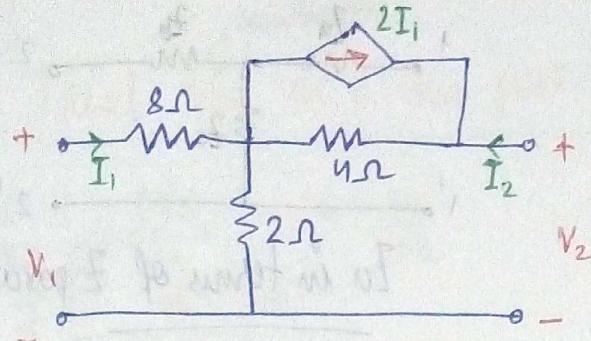


Get [Y].

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

$$* Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}$$
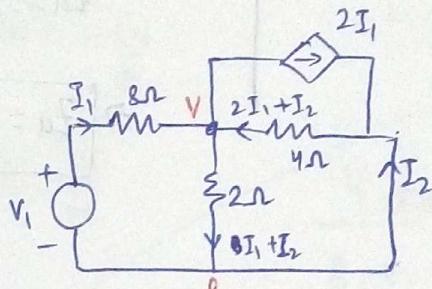
$$= \frac{I_1}{20/3 I_1} = \left(\frac{3}{20}\right)$$



$$V_0 = 2(I_1 + I_2)$$

$$= V_1 - 8I_1$$

$$= -4(2I_1 + I_2)$$

$$2I_1 + 2I_2 = -8I_1 - 4I_2$$

$$10I_1 = -6I_2$$

$$\boxed{5I_1 = -3I_2}$$


$$V_1 - 8I_1 = 2\left(I_1 - \frac{5}{3}I_1\right)$$

$$V_1 - 8I_1 = -\frac{4}{3}I_1$$

$$V_1 = \left(\frac{8-4}{3}\right)I_1 = \frac{20}{3}I_1$$

$$* Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0}$$
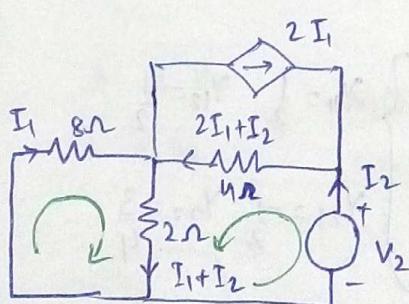
$$= \frac{I_1}{-20I_1} = \left(-\frac{1}{20}\right)$$



$$* Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0}$$

$$= \frac{-5I_1}{-20I_1} = \left(\frac{1}{4}\right)$$

$$8I_1 + 2(I_1 + I_2) = 0$$


$$10I_1 = -2I_2$$

$$\Rightarrow I_2 = -5I_1$$

$$V_2 = 4(2I_1 + I_2) + 2(I_1 + I_2)$$

$$V_2 = 10I_1 + 6I_2$$

$$V_2 = 10I_1 - 30I_1 = -20I_1$$

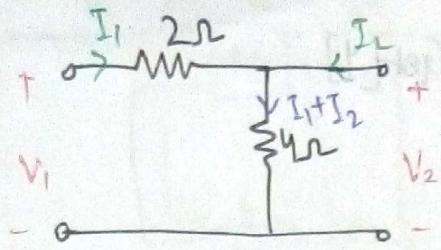

$$[Z] = ?$$

$$[Y] = ?$$

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

$$V_1 - 2I_1 - 4(I_1 + I_2) = 0$$

$$\begin{cases} V_1 = 6I_1 + 4I_2 \\ V_2 - 4(I_1 + I_2) = 0 \end{cases} \quad \begin{array}{l} Z_{11} = 6 \\ Z_{12} = 4 \\ Z_{21} = 4 \\ Z_{22} = 4 \end{array}$$

$$V_1 - V_2 = 2I_1$$


$$\Rightarrow I_1 = \frac{1}{2}V_1 - \frac{1}{2}V_2$$

$$4I_2 = V_1 - 6I_1 = V_1 - (2V_1 - 3V_2)$$

$$I_2 = -\frac{1}{2}V_1 + \frac{3}{4}V_2$$

$$[Z] = \begin{bmatrix} 6 & 4 \\ 4 & 4 \end{bmatrix} \text{ and}$$
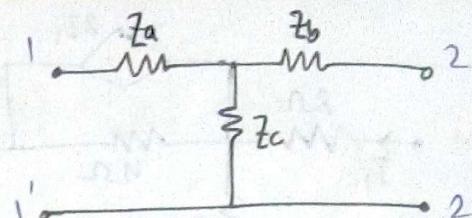
$$[Y] = \begin{bmatrix} \frac{1}{2} & -\frac{1}{2} \\ -\frac{1}{2} & \frac{3}{4} \end{bmatrix}$$




Za in terms of Z parameters

$$Z_{11} = Z_a + Z_c \quad Z_{12} = Z_c$$

$$Z_{21} = Z_c \quad Z_{22} = Z_b$$

$$Z_a = Z_{11} - Z_{12}$$

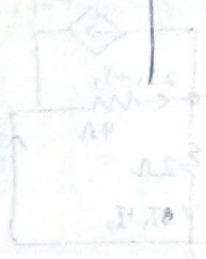

$$\left(\frac{1}{N}\right) = \frac{Z_a R}{(Z_a + Z_c)R}$$

$$0 = N \left| \frac{1}{N} \right| = \frac{1}{N}$$


$$\left(\frac{1}{N}\right) = \frac{1}{N}$$

$$0 = N \left| \frac{1}{N} \right| = \frac{1}{N}$$

$$\left(\frac{1}{N}\right) = \frac{1}{N}$$

$$\frac{1}{N} = \frac{1}{Z_b}$$

Ideal t_{fo} as a two port network

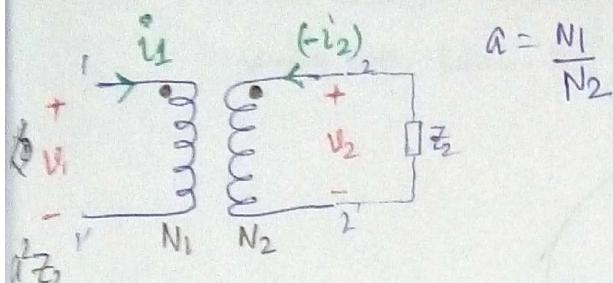

$$a = \frac{N_1}{N_2}$$

$$\frac{v_1}{N_1} = \frac{v_2}{N_2}$$

$$N_1 i_1 = N_2 (-i_2)$$

or $v_1 = a v_2$
 $i_1 = -\frac{i_2}{a}$

$$\begin{bmatrix} v_1 \\ i_1 \end{bmatrix} = \begin{bmatrix} a & 0 \\ 0 & -1/a \end{bmatrix} \begin{bmatrix} v_2 \\ i_2 \end{bmatrix}$$

Power Input to the System = $v_1 i_1 + v_2 (-i_2) = 0$

$$Z_2 = \frac{v_2}{i_2}$$


$$\frac{v_1}{i_1} = \frac{a v_2}{(-i_2/a)} = -a^2 Z_2$$

4 elements (fundamental)

R, L, C, IT

(See Next Page)


(ideal t_{fo})

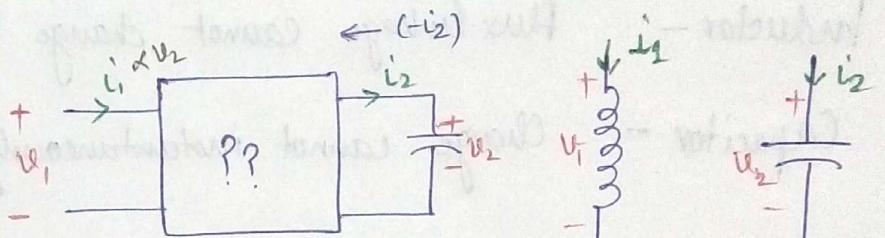

$v_1 = +k_1 i_2$
 $i_1 = k_2 v_2$ Tellingen

$$\begin{bmatrix} v_1 \\ i_1 \end{bmatrix} = \begin{bmatrix} 0 & -k_1 \\ k_2 & 0 \end{bmatrix} \begin{bmatrix} v_2 \\ i_2 \end{bmatrix}$$

$(k_1 \neq k_2)$

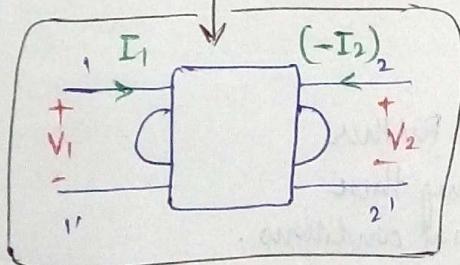

$$\begin{bmatrix} v_1 \\ i_1 \end{bmatrix} = \begin{bmatrix} 0 & K \\ \frac{1}{K} & 0 \end{bmatrix} \begin{bmatrix} v_2 \\ i_2 \end{bmatrix}$$

$$i_1 \propto v_2 \\ v_1 \propto i_2 \Rightarrow \frac{v_1(s)}{i_1(s)} = K \frac{i_2(s)}{v_2(s)} = \frac{K}{1/s} = K s$$

$$i_1 = \frac{1}{L} \int_{-\infty}^t v_1 dt$$

$$v_2 = \frac{1}{C} \int_{-\infty}^t i_2 dt$$


Power $\rightarrow v_1 i_1 + v_2 (-i_2) = 0$.

* Non-Reciprocal Network

(It will not follow Reciprocity Thm)

* If a resistance is connected at 2-2', we get a resistance only at 1-1'

* Capacitor \rightarrow Inductor at

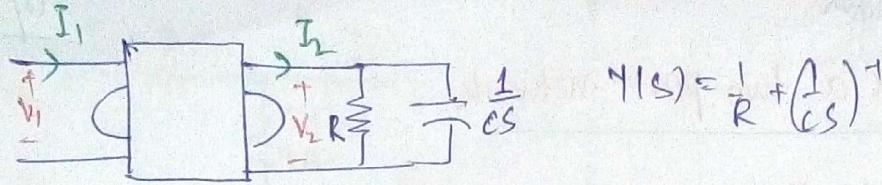


List of 5 fundamental elements:-

R, L, C, Ideal t_{fo} , Gyrator.


Lossless

* Inductor - flux linkage cannot change instantaneously

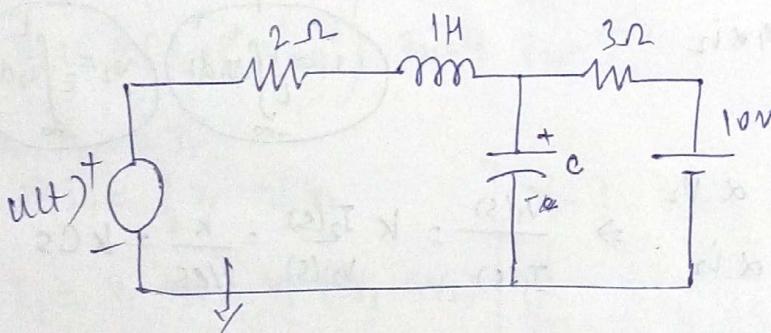
Capacitor - charge cannot instantaneously




$t < 0$

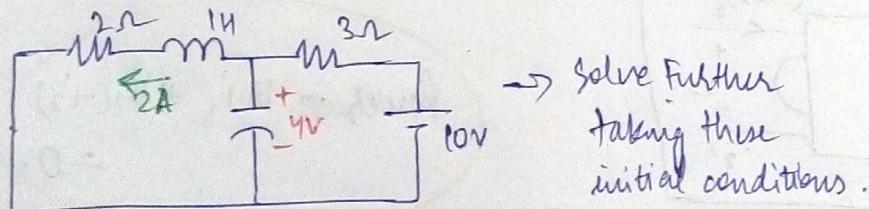

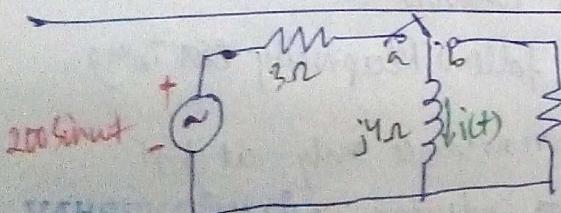* Statements of Theorems can come in exam).


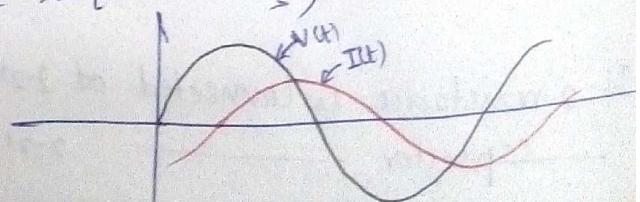
$$i(t) = \frac{200}{5} \sin\left(\omega t - \tan^{-1}\frac{4}{3}\right)$$



If switch is connected to b from a in 0 time gap,

we cannot directly tell the current through inductor until and unless we know the time at which switching happened.