
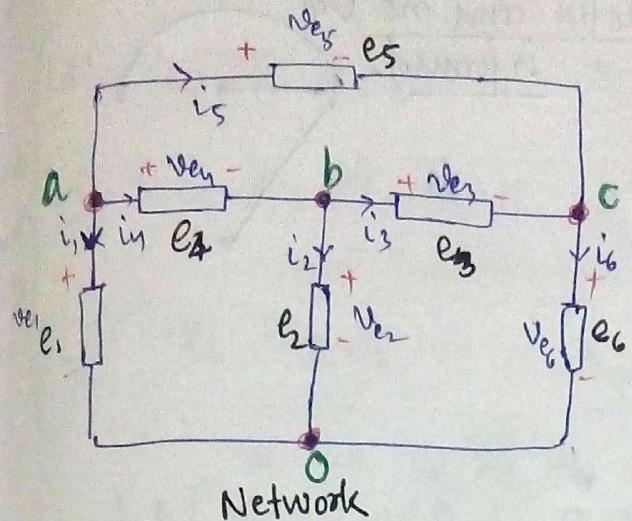


Graph Theory Applied to Network Analysis

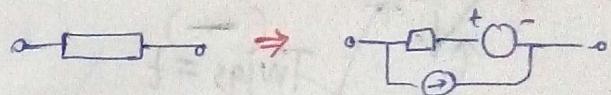

Elements:-



Directed Graph

KCL at node A:-

$$ie_1 + ie_4 + ie_5 = 0$$

node b:-

$$ie_2 + ie_3 - ie_4 = 0$$

node c:-

$$i_{eg} - i_{es} - i_{eg} = 0$$

~~extra~~ \rightarrow node 0 :-

$$-(ie_1 + ie_2 + ie_6) = 0$$

This can be manufactured from linear combination of above 3 equations.
So, we usually don't write it.

i₁, i₂, i₃, i₄, i₅, i₆


$$\begin{array}{l}
 \text{KCLata} : \left[\begin{array}{cccccc} 1 & 0 & 0 & 1 & 1 & 0 \end{array} \right] \left[\begin{array}{c} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \end{array} \right] = \left[\begin{array}{c} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{array} \right] \\
 \text{KCLarb} : \left[\begin{array}{cccccc} 0 & 1 & 1 & -1 & 0 & 0 \end{array} \right] \left[\begin{array}{c} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \end{array} \right] = \left[\begin{array}{c} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{array} \right] \\
 \text{KCLatc} : \left[\begin{array}{cccccc} 0 & 0 & -1 & 0 & -1 & 1 \end{array} \right] \left[\begin{array}{c} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \end{array} \right] = \left[\begin{array}{c} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{array} \right] \\
 \text{KCLato} : \left[\begin{array}{cccccc} -1 & -1 & 0 & 0 & 0 & -1 \end{array} \right] \left[\begin{array}{c} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \end{array} \right] = \left[\begin{array}{c} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{array} \right]
 \end{array}$$

at any node,
arrow away $\Rightarrow +$

$$[A] [e] = [0]$$

$$[A]^T [v_N] = [v_e]$$


Tree of Graph

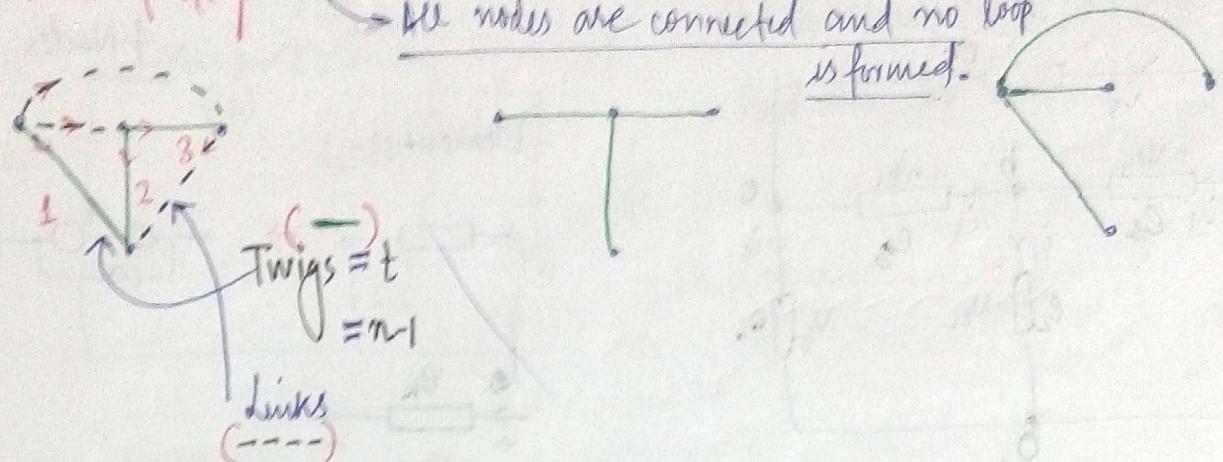


$n \rightarrow$ nodes $\text{No. of twigs} = t = n-1$

$e \rightarrow$ edges No. of links
 $= \text{No. of edges} - \text{twigs} = e-t$


$$= e-n+1$$

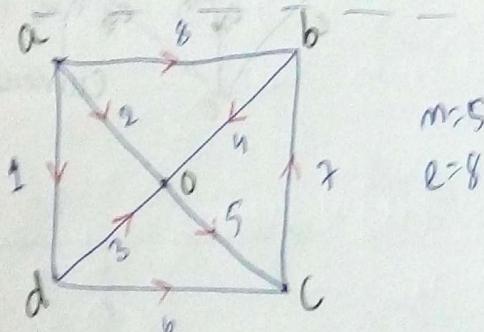
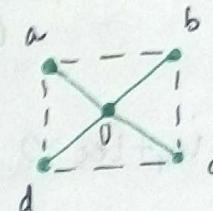
$$\begin{matrix} n: 5 \\ e: 8 \end{matrix}$$



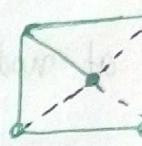
$$\begin{matrix} t = 4 \quad (n-1) \\ e = 4 \quad (e-t) \end{matrix}$$



Q)

i_a i_b i_c i_d i_a i_b i_c i_d.
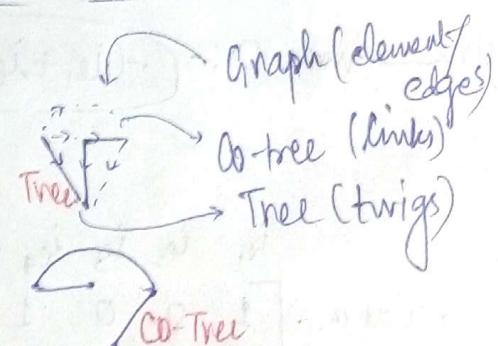
$$= \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 0 & 0 & 1 \\ 0 & 0 & 0 & 1 & 0 & 0 & -1 & -1 \\ 0 & 0 & 0 & 0 & -1 & -1 & 1 & 0 \\ -1 & 0 & -1 & 0 & 0 & 1 & 0 & 0 \end{bmatrix}$$



Relationship between node voltages and element voltages

$$V_{ao} = V_{e_1}$$

$$V_{bo} = V_{e_2}$$

$$V_{co} - V_{eo} = V_{e_3}$$

$$[A]^T [v_N] = [v_e]$$

$$[V_{ao} \quad V_{bo} \quad V_{eo}]^T \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 1 & -1 \\ 1 & -1 & 0 \\ 1 & 0 & -1 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} V_{e_1} \\ V_{e_2} \\ V_{e_3} \\ V_{e_4} \\ V_{e_5} \\ V_{e_6} \end{bmatrix}$$

ex1

$(n-1)$

Loop Analysis

$$\begin{array}{c} 1 \\ | \\ \sqrt[3]{2} \\ | \\ 6 \end{array}$$


- L4: $v_{e_1} + v_{e_2} - v_e = 0$ 
 L5: $v_{e_5} - v_{e_3} + v_{e_2} - v_e = 0$ 
 L6: $v_{e_6} - v_{e_2} + v_{e_3} = 0$ 

$$\begin{array}{l}
 L4 \\
 L5 \\
 L6
 \end{array}
 \left[\begin{array}{cccccc} v_{e_1} & v_{e_2} & v_{e_3} & v_{e_4} & v_{e_5} & v_{e_6} \\ -1 & 1 & 0 & 1 & 0 & 0 \\ -1 & 1 & -1 & 0 & 1 & 0 \\ 0 & -1 & 1 & 0 & 0 & 1 \end{array} \right]
 \left[\begin{array}{c} v_{e_1} \\ v_{e_2} \\ v_{e_3} \\ v_{e_4} \\ v_{e_5} \\ v_{e_6} \end{array} \right] = \left[\begin{array}{c} 0 \\ 0 \\ 0 \\ 0 \end{array} \right]$$

$[B] [v_e] = [0]$

Graph Theory - in Network Analysis

27/10/16

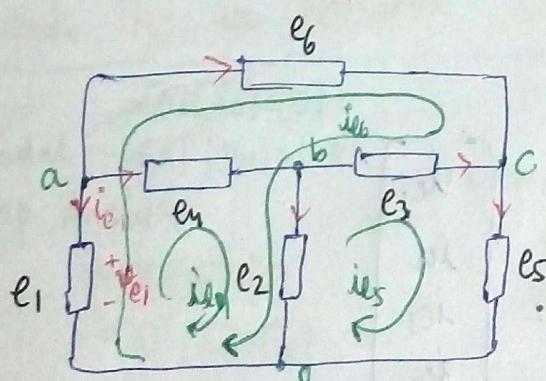

Let n = total no. of nodes
 e = total no. of elements

$$[i_e] = \begin{bmatrix} i_{e_1} \\ i_{e_2} \\ \vdots \\ i_{e_6} \end{bmatrix}$$


KCL at nodes:-

Nodal Analysis


$$[A] [i_e] = [0]$$

\downarrow


$(n-1)e$ $e-1$

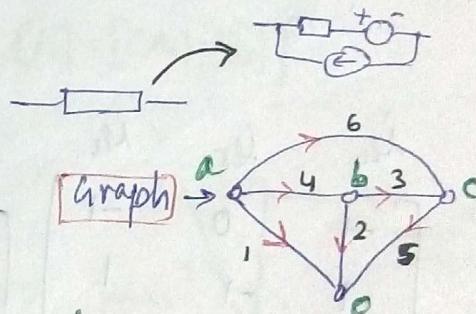

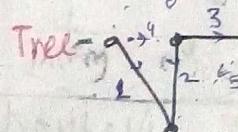Tree \rightarrow Subset of graph where all the nodes are shown but only selected edges are shown.



$$\text{Twigs} = t = n-1$$

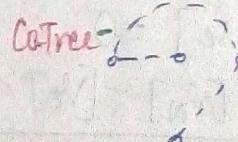

$$\begin{aligned}
 \text{Links} &= l = e - t \\ &= e - n + 1
 \end{aligned}$$

Nodal
Analysis

{ Relationship of node voltages with element voltages

$$[A]^T [v_N] = [v_e]$$

$e \times (n+1)$ $(n+1) \times 1$ 1×1

Loops dictated by links are called fundamental loops.

KVL in the F-loops:-

$$L4: v_{e_4} + v_{e_2} - v_{e_1} = 0$$

$$L5: v_{e_5} - v_{e_2} + v_{e_3} = 0$$

$$L6: v_{e_6} - v_{e_3} + v_{e_2} - v_{e_1} = 0$$

Links \rightarrow Funda.
loop.

$$[B] [v_e] = [0]$$

$n \times n+1$ $(n+1) \times 1$ 1×1

(Move along direction of arrow $\Rightarrow +$)

$$\begin{bmatrix} v_1 & v_2 & v_3 & v_4 & v_5 & v_6 \end{bmatrix} = \begin{bmatrix} v_{e_1} \\ v_{e_2} \\ v_{e_3} \\ v_{e_4} \\ v_{e_5} \\ v_{e_6} \end{bmatrix}$$

* Relating loop currents $[i_e]$ with element currents $[i_e]$

$$i_{e_1} = -i_{e_4} - i_{e_6}$$

$$i_{e_2} = i_{e_6} - i_{e_5} + i_{e_4}$$

$$\begin{bmatrix} i_{e_1} & i_{e_2} & i_{e_3} \\ -1 & 0 & -1 \\ 1 & -1 & 1 \\ 0 & 1 & -1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} i_{e_4} \\ i_{e_5} \\ i_{e_6} \end{bmatrix} = \begin{bmatrix} i_{e_1} \\ i_{e_2} \\ i_{e_3} \\ i_{e_4} \\ i_{e_5} \\ i_{e_6} \end{bmatrix}$$

$$[B]^T [i_e] = [i_e]$$

$(n+1) \times n+1$ 1×1

Nodal Method



$$\rightarrow [A][i_e] = 0$$

$$\rightarrow [A]^T [v_N] = [v_e]$$

Loop Analysis

$$\rightarrow [B][v_e] = 0$$

$$\rightarrow [B]^T [i_e] = [i_e]$$

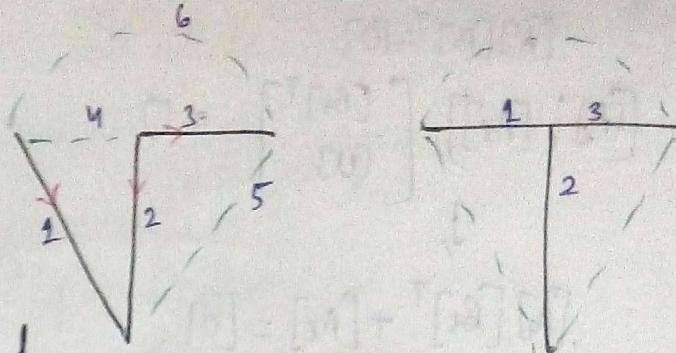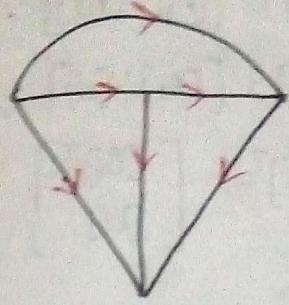

$$[A] = \begin{bmatrix} t & l \\ 1 & 2 & 3 & 4 & 5 & 6 \\ a & 1 & 0 & 0 & 1 & 1 & 0 & 1 \\ b & 0 & 1 & 1 & -1 & 0 & 0 \\ c & 0 & 0 & -1 & 0 & 1 & -1 \end{bmatrix}$$

$$[A] = \begin{bmatrix} [A_t] & [A_L] \\ l \times t & t \times l \end{bmatrix}$$

$$[B] = \begin{bmatrix} [B_t] & [B_L] \\ l \times t & t \times l \end{bmatrix}$$

31/10/16

Graph Th. in Network Analysis

$$[A] = \begin{bmatrix} [A_t] & [A_L] \end{bmatrix}$$

Nodal
Loop Analysis
Cut-set Analysis?


$$[A][i_e] = [0]$$

$$[A]^T [v_n] = [v_e]$$


$$[B][v_e] = [0]$$

$$[B]^T [i_e] = [i_e]$$

$$[B_t]^T = -[A_t]^{-1}[A_L]$$

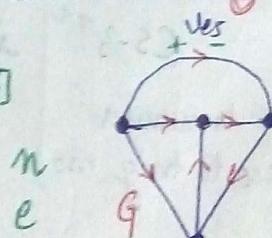
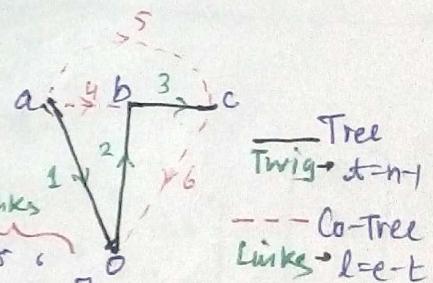
$$[A] = \begin{bmatrix} 1 & 0 & 0 & 1 & 1 & 0 \\ 0 & -1 & 1 & -1 & 0 & 0 \\ 0 & 0 & -1 & 0 & -1 & 1 \end{bmatrix}$$



Loop Method :-

* $[A]$ and $[B]$ are orthogonal matrices.

$$[A][B]^T = [0]$$

$$[B][v_e] = [0]$$

$$\begin{bmatrix} v_1 & v_2 & v_3 & v_4 & v_5 & v_6 \\ L_1 & -1 & -1 & 0 & 1 & 0 & 0 \\ L_2 & -1 & -1 & -1 & 0 & 1 & 0 \\ L_3 & 0 & 1 & 1 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} v_{e_1} \\ v_{e_2} \\ v_{e_3} \\ v_{e_4} \\ v_{e_5} \\ v_{e_6} \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}$$

Not necessarily
sq matrix.

$$[B_t] \quad l \times t$$

$$[B_L] = [I] = I_{n-3} \quad n \times l$$

$n \times l$ unitary matrix.

BANUBHAV
JAIN
NOTES

$$[A][B]^T = [0]$$

$$[A_E] \begin{bmatrix} [A_U] \\ [A_L] \end{bmatrix} \begin{bmatrix} [B_E]^T \\ [U] \end{bmatrix} = 0$$

$$[A_E][B_E]^T + [A_U] = [0]$$

$$\therefore [B_E]^T = -[A_U]^{-1}[A_E]$$

$$[B_E] = \{ \quad \}^T$$


$$[A] = [[A_U], [A_E]]$$

$$[B] = [[B_E]; [U]]$$

$$[B]^T = \left[\begin{array}{c} [B_E]^T \\ [U] \end{array} \right]$$

* Loops formed by links are called fundamental loops.

Cut Set Method & Analysis of networks

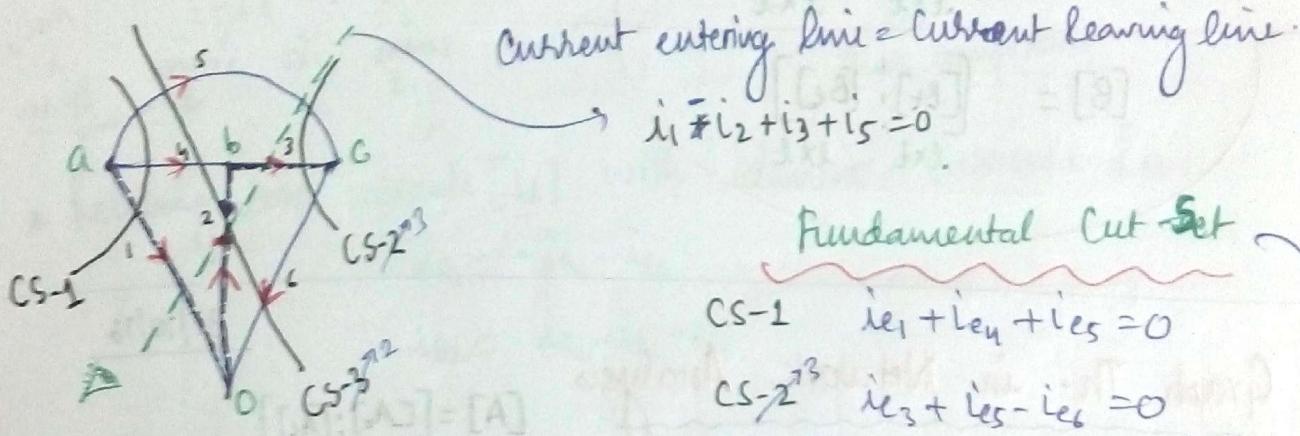

Fundamental Cut Set

$$CS-1 \quad i_{e_1} + i_{e_4} + i_{e_5} = 0$$

$$CS-2 \quad i_{e_3} + i_{e_5} - i_{e_6} = 0$$

$$CS-3 \quad i_{e_2} + i_{e_4} + i_{e_5} = i_{e_6}$$

It's better to number cutset acc to twigs no.


A cut including exactly one twig

$$\begin{array}{ccccccc|c} & i_{e_1} & i_{e_2} & i_{e_3} & i_{e_4} & i_{e_5} & i_{e_6} & \\ CS-1 & 1 & 0 & 0 & 1 & 1 & 0 & \begin{bmatrix} i_{e_1} \\ i_{e_2} \\ i_{e_3} \\ i_{e_4} \\ i_{e_5} \\ i_{e_6} \end{bmatrix} \\ CS-2 & 0 & 0 & 1 & 0 & 1 & -1 & = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix} \\ CS-3 & 0 & 1 & 0 & 1 & 1 & -1 & \end{array}$$

$$[Q]$$

$$\begin{bmatrix} 1 & 0 & 0 & | & 1 & 1 & 0 \\ 0 & 1 & 0 & | & 1 & 1 & -1 \\ 0 & 0 & 1 & | & 0 & 1 & -1 \end{bmatrix}$$

$$[[Q_{st}]_{+xk}, [Q_{st}]_{+x0}] = [u]; [Q_{st}]$$

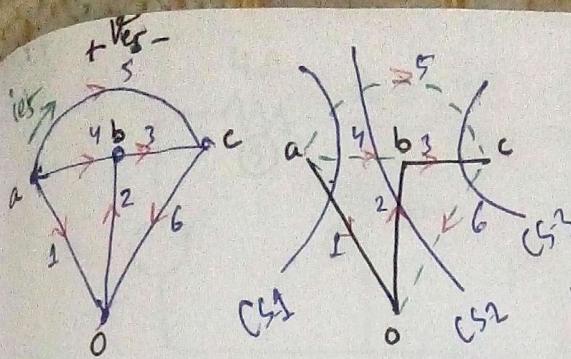Summary :-

$$\text{Nodal: } [A][i_e] = [0]$$

$$[A^T]^T [v_{et}] = [i_e]$$

$$\text{Loop: } [B][v_e] = [0]$$

$$[B]^T [i_e] = [i_e]$$

$$[A][B]^T = [0] \quad \therefore \text{Orthogonal}$$

$$[B_t]^T = -[A_t]^{-1}[A_e]$$

$$i_e = \begin{bmatrix} i_{e1} \\ i_{e2} \\ i_{e3} \end{bmatrix} \quad [v_{et}] = \begin{bmatrix} v_{e1} \\ v_{e2} \\ v_{e3} \end{bmatrix}$$

Cutset :-

Write down KCLs at the cut sets.

$$CS_1 \quad i_{e1} + i_{e2} + i_{e3} = 0$$


$$CS_2 \quad i_{e2} + i_{e3} + i_{e4} = i_{e6}$$

$$CS_3 \quad i_{e3} + i_{e5} = i_{e6}$$

$$CS_1 \quad \begin{bmatrix} 1 & 0 & 0 & 1 & 1 & 0 \end{bmatrix} \begin{bmatrix} i_{e1} \\ i_{e2} \\ i_{e3} \\ i_{e4} \\ i_{e5} \\ i_{e6} \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}$$

$$CS_2 \quad \begin{bmatrix} 0 & 1 & 0 & 1 & 1 & -1 \end{bmatrix} \begin{bmatrix} i_{e1} \\ i_{e2} \\ i_{e3} \\ i_{e4} \\ i_{e5} \\ i_{e6} \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}$$

$$CS_3 \quad \begin{bmatrix} 0 & 0 & 1 & 0 & 1 & -1 \end{bmatrix} \begin{bmatrix} i_{e1} \\ i_{e2} \\ i_{e3} \\ i_{e4} \\ i_{e5} \\ i_{e6} \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}$$

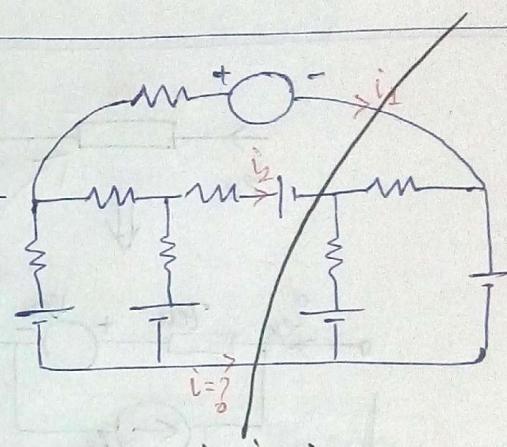Example
of cutset:-

$$i_1 + i_2 + i_3 = 0$$

$$\Rightarrow i = -i_1 - i_2$$

$$[Q][i_e] = [0]$$

$$[Q] = [[U]; [Q_e]]$$

$[Q_t]$

$$v_{e1t} + v_{e2t} = v_{e4}$$

$$\begin{bmatrix} v_{e1t} & v_{e2t} & v_{e3t} \\ 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ 1 & 1 & 0 \\ 1 & 1 & 1 \\ 0 & -1 & -1 \end{bmatrix} \begin{bmatrix} v_{e1t} \\ v_{e2t} \\ v_{e3t} \end{bmatrix} = \begin{bmatrix} v_{e1} \\ v_{e2} \\ v_{e3} \\ v_{e4} \\ v_{e5} \\ v_{e6} \end{bmatrix}$$

$$[Q]^T [v_{et}] = [v_e]$$

* $[B]$ & $[Q]$ are orthogonal.

$$[B][Q]^T = [0]$$

$$[[B_t]; [U]] [[U]; [Q_e]]^T = [0]$$

$$[[B_L][V]] \begin{bmatrix} [V] \\ [Q_L]^T \end{bmatrix} = [0]$$


$$[B_L] + [Q_L]^T = [0]$$

$$\Rightarrow [B_L] = -[Q_L]^T$$

$$[B_L]^T = -[Q_L]$$

$$-[A_L]^{-1}[A_L] = -[Q_L]$$

$$\Rightarrow [Q_L] = [A_L]^{-1}[A_L]$$

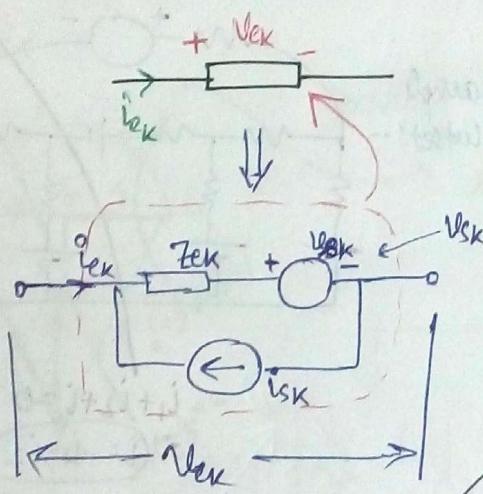

For K^{th} element

by Loop analysis:-

$$V_{ek} = V_{sk} + Z_{ek}(i_{ek} + i_{sk})$$

$$\text{or } V_{ek} = Z_{ek}i_{ek} + V_{sk} + Z_{ek}i_{sk}$$

$$\begin{bmatrix} V_1 \\ V_2 \\ \vdots \\ V_6 \end{bmatrix} = \begin{bmatrix} Z_{11} & 0 & \dots & 0 \\ 0 & Z_{22} & \dots & 0 \\ \vdots & \vdots & \ddots & \vdots \\ 0 & 0 & \dots & Z_{66} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ \vdots \\ i_6 \end{bmatrix} + \begin{bmatrix} V_{s1} \\ V_{s2} \\ \vdots \\ V_{s6} \end{bmatrix} + \begin{bmatrix} Z_{11} & 0 & \dots & 0 \\ 0 & Z_{22} & \dots & 0 \\ \vdots & \vdots & \ddots & \vdots \\ 0 & 0 & \dots & Z_{66} \end{bmatrix} \begin{bmatrix} i_{s1} \\ i_{s2} \\ \vdots \\ i_{s3} \end{bmatrix}$$

diagonal matrix

$$[V_e] = [Z_e][i_e] + [V_s] + [Z_e][i_s]$$


Premultiply both sides by $[B]$

$$\Rightarrow [B][V_e] = [B][Z_e][i_e] + [B][V_s] + [B][Z_e][i_s] = [0]$$

$$[B][Z_e][i_e] = -[B][V_s] - [B][Z_e][i_s]$$

$$[B][Z_e][B]^T[i_e] = -[B][V_s] - [B][Z_e][i_s]$$



Z_{loop}

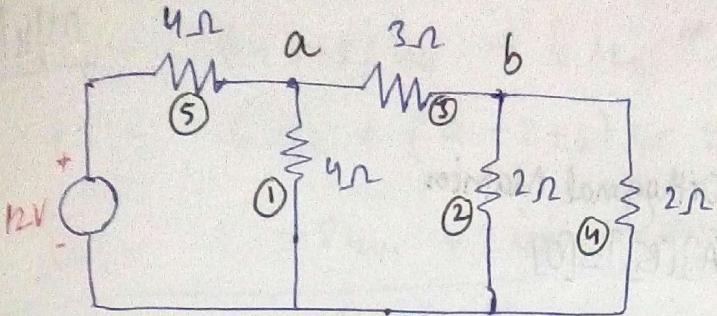

By loop analysis

$$\begin{bmatrix} v_{11} & v_{12} & v_{13} & v_{14} & v_{15} \\ -1 & -1 & 1 & 0 & 0 \end{bmatrix} = [B]$$
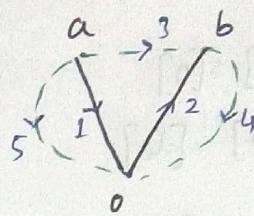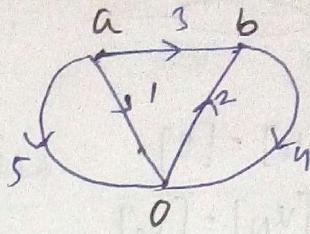
$$\begin{bmatrix} l_4 & 0 & 1 & 0 & 1 \\ 0 & 1 & 0 & 1 & 0 \\ -1 & 0 & 0 & 0 & 1 \end{bmatrix} = [B]$$




$$[Z_e] = \begin{bmatrix} 4 & 0 & 0 & 0 & 0 \\ 0 & 2 & 0 & 0 & 0 \\ 0 & 0 & 3 & 0 & 0 \\ 0 & 0 & 0 & 2 & 0 \\ 0 & 0 & 0 & 0 & 4 \end{bmatrix}$$

$$[Y_e] = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 1/2 \end{bmatrix}$$

$$[i_s] = [0]$$

By nodal method

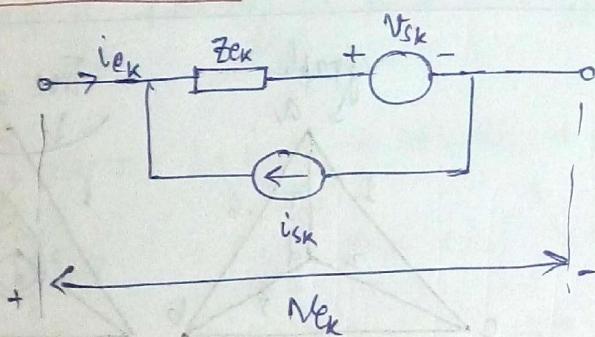

$$i_{ek} + i_{sk} = \frac{v_{ek} - v_{sk}}{z_{ek}}$$

$$= Y_{ek} v_{ek} - Y_{ek} v_{sk}$$

$$\Rightarrow i_{ek} = Y_{ek} v_{ek} - i_{sk} - Y_{ek} v_{sk}$$

$$[i_e] = [Y_e] [v_e] - [i_s] - [Y_e] [v_s]$$


Premultiply both sides by $[A]$.

$$\Rightarrow [A][i_e] = [A][Y_e][v_e] - [A][i_s] - [A][Y_e][v_s] = [0]$$

$$[A][Y_e][v_e] = \underbrace{[A][i_s]}_{[A][i_s]} + [A][Y_e][v_s]$$

$$[A][Y_e][A]^T[v_N] = [A][i_s] + [A][Y_e][v_s]$$
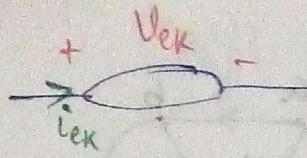
$$[A] = \begin{bmatrix} 1 & 2 & 3 & 4 & 5 \\ 1 & 0 & 1 & 0 & 1 \\ 0 & -1 & -1 & 1 & 0 \end{bmatrix}$$



Nodal

$$[A][i_e] = [0]$$

$$[A]^T [v_N] = [v_e]$$

Mesh

$$[B][v_e] = [0]$$

$$[B]^T [i_e] = [i_e]$$

Cut-set


$$[Q][i_e] = [0]$$

$$[Q]^T [v_{et}] = [v_e]$$

Orthogonal Matrices

$$\rightarrow [A][B]^T = [0]$$




$$\rightarrow [B][Q]^T = [0]$$

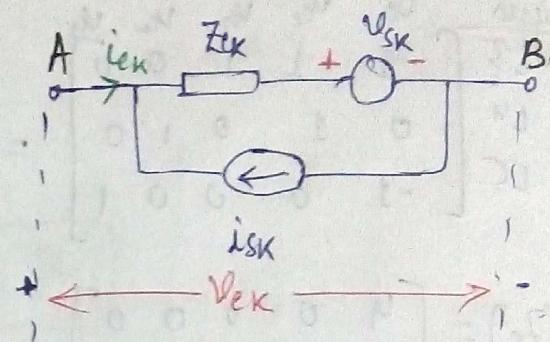

$$\text{Nodal } [A][Y][A]^T [v_N] = [A][i_s] + [A][Y][v_s]$$

$$\text{Cut-set } [Q][Y][Q]^T [v_N] = [Q][i_s] + [Q][Y][v_s]$$
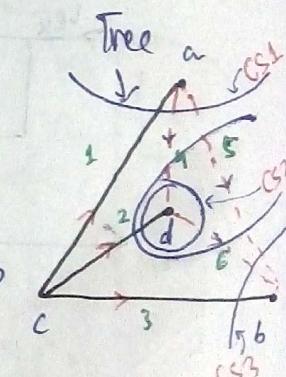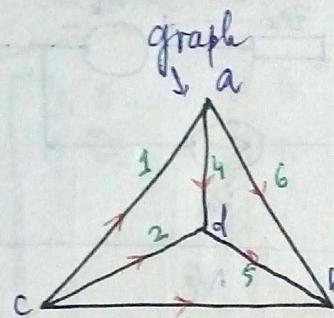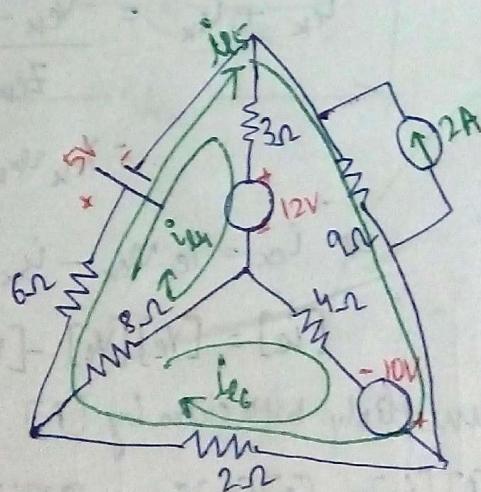
$$\text{Loop } [B][Z][B]^T [i_e] = -[B][v_s] - [B][Z][i_s]$$



Mesh Analysis

$$[v_s] = \begin{bmatrix} 5 \\ 0 \\ 0 \\ 12 \\ 0 \\ -10 \end{bmatrix}$$

$$[i_s] = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 2 \\ 0 \end{bmatrix}$$

$$[Z] = \begin{bmatrix} 6 & 0 & 0 & 0 & 0 & 0 \\ 0 & 8 & 0 & 0 & 0 & 0 \\ 0 & 0 & 2 & 0 & 0 & 0 \\ 0 & 0 & 0 & 3 & 0 & 0 \\ 0 & 0 & 0 & 0 & 9 & 0 \\ 0 & 0 & 0 & 0 & 0 & 4 \end{bmatrix}$$

$$[B] = \begin{bmatrix} 1 & -1 & 0 & 1 & 0 & 0 \\ 1 & 0 & -1 & 0 & 1 & 0 \\ 0 & 1 & -1 & 0 & 0 & 1 \end{bmatrix}$$


C. S. Sunday
13/11/16
fisher

$$L4: - (6+3+8)i_{L_4} + 6i_{L_5} - 8i_{L_6} = -5-12$$

$$L5: - 6i_{L_4} + (9+2+6)i_{L_5} + 2i_{L_6} = -5$$

$$L6: - -8i_{L_4} + 2i_{L_5} + (8+4+2)i_{L_6} = +10$$
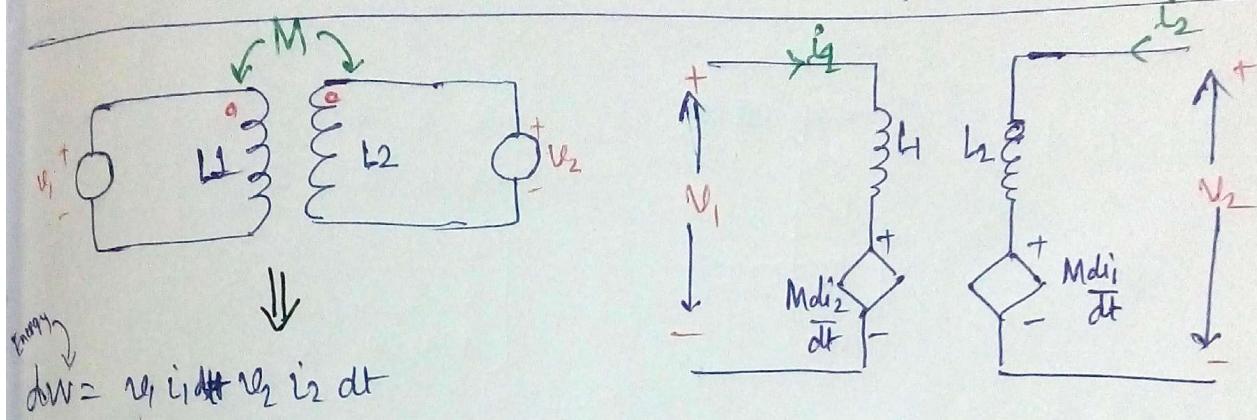
$$Q = ? = CS_1 \begin{bmatrix} i_{e_1} & i_{e_2} & i_{e_3} & i_{e_4} & i_{e_5} & i_{e_6} \\ -1 & 0 & 0 & +1 & 1 & 0 \\ 0 & -1 & 0 & -1 & 0 & 1 \\ 0 & 0 & -1 & 0 & -1 & -1 \end{bmatrix}$$



$$dW = \left(L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \right) i_1 dt + \left(L_2 \frac{di_2}{dt} + M \frac{di_1}{dt} \right) i_2 dt$$

$$dW = L_1 i_1 di_1 + M i_1 di_2 + L_2 i_2 di_2 + M i_2 di_1$$

$$\int_0^t dW = L_1 \int_0^t i_1 di_1 + L_2 \int_0^t i_2 di_2 + M \int_0^t d(i_1 i_2)$$

$$W = \frac{1}{2} L_1 i_1^2(t) + \frac{1}{2} L_2 i_2^2(t) + M i_1(t) i_2(t)$$