

DISCRETE TIME FOURIER TRANSFORM

26/09/16





$$A: X(e^{j\omega}) = \sum_{n=-\infty}^{\infty} x[n] e^{-jn\omega}$$

$$S: x[n] = \frac{1}{2\pi} \int_{-\pi}^{\pi} X(e^{j\omega}) e^{j\omega n} d\omega$$

$$X(e^{j(\omega+2\pi)}) = X(e^{j\omega})$$

$$F \rightarrow (0, 1, \dots 10^8 - 10^6, \dots) \text{ Hz}$$
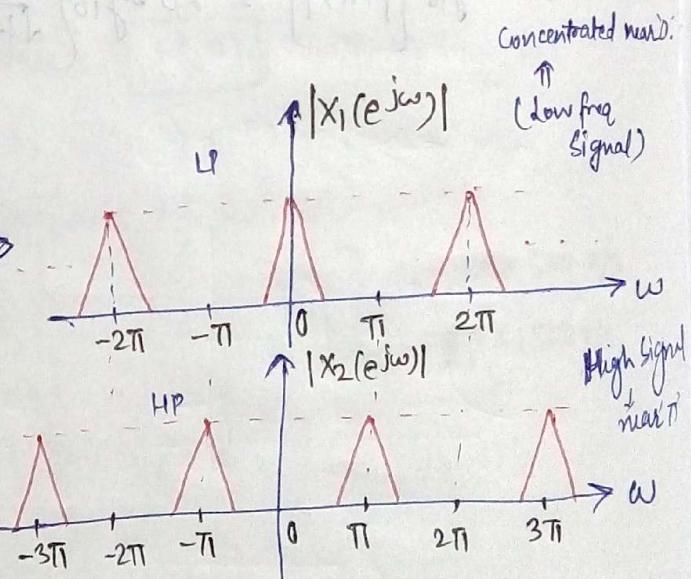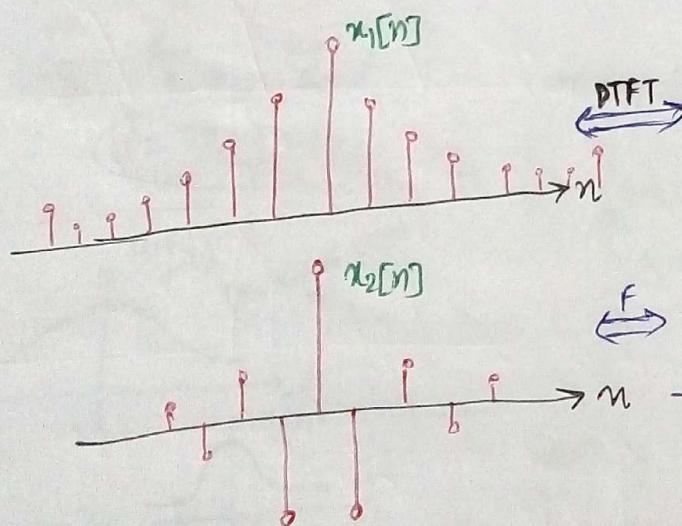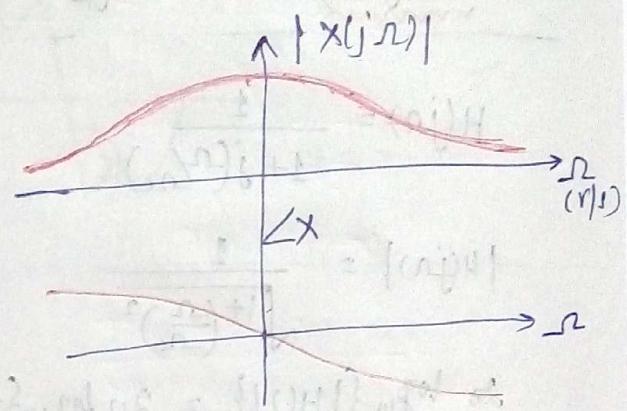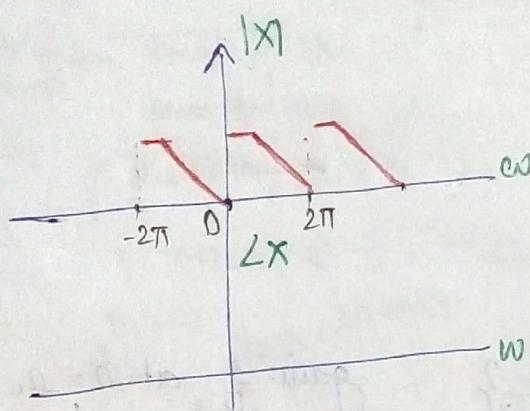
$$\omega \rightarrow 2\pi f \quad \text{r/s.}$$



$$x_1[n] = \{1, 1, 1, \dots\} \quad \text{or} \quad x_1[n] = \{1, a, a^2, \dots\} \quad |a| > 0$$

$$x_2[n] = \{1, -1, 1, -1, \dots\} \quad \text{or} \quad x_2[n] = \{1, a, a^2, \dots\} \quad -1 < a < 0$$


$$X_1(e^{j\omega}) = ?$$

$$X_2(e^{j\omega}) = ?$$

$$x[n] = a^n u[n]$$


$$|a| < 1$$
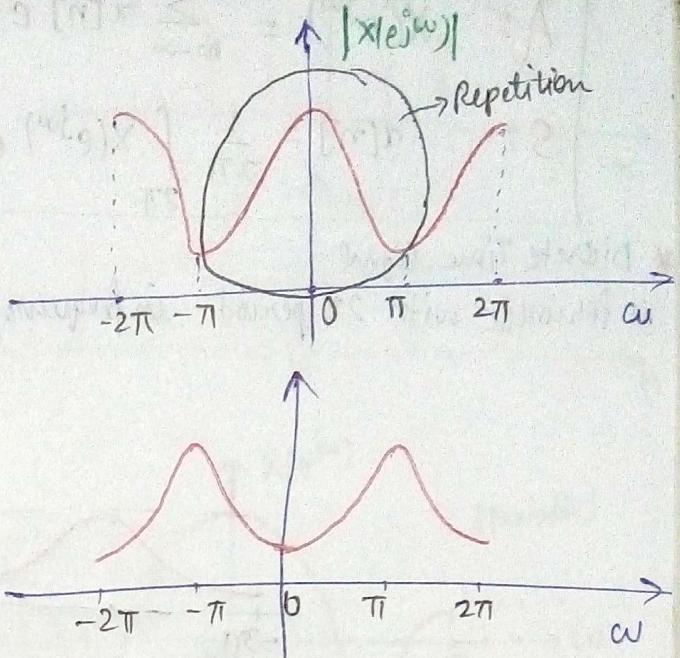
$$X(e^{j\omega}) = \frac{1}{1 - ae^{-j\omega}}$$



* In some transforms, energy is lost

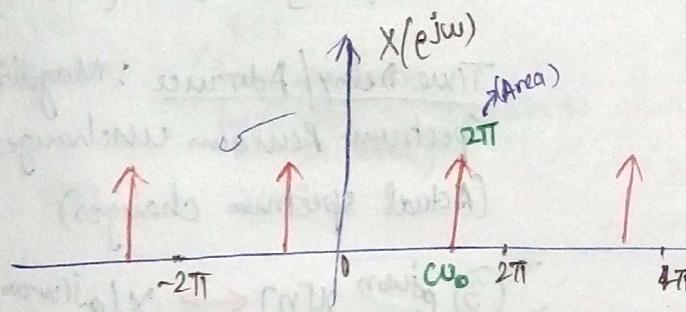\Rightarrow They are not reproducible back to original form.



$$X(e^{j\omega}) = 2\pi \sum_{l=-\infty}^{\infty} \delta(\omega - \omega_0 - 2\pi l)$$

$$x[n] = \frac{1}{2\pi} \int_{-\pi}^{\pi} X(e^{j\omega}) e^{j\omega n} d\omega$$

$$\begin{aligned} &= \frac{1}{2\pi} \int_{-\pi}^{\pi} \delta(\omega - \omega_0 - 2\pi l) e^{j\omega n} d\omega \\ &= e^{j\omega_0 n} \cdot e^{j2\pi ln} \\ &= e^{j\omega_0 n} \end{aligned}$$

$$x[n] = \sum_{k=0}^{N-1} G_k e^{j k \left(\frac{2\pi}{N}\right) n}$$

$2\pi \rightarrow$ divided into 'N' points.

$$\text{Let } N=8 \quad \omega_0 = \frac{2\pi}{8} \times 0$$

$$\omega_1 = \frac{2\pi}{8} \times 1$$

$$\omega_8 = \frac{2\pi}{8} \times 8$$


$$X(e^{j\omega}) = \sum_{k=-\infty}^{\infty} 2\pi G_k \delta(\omega - 2\pi \frac{k}{N})$$

A: $X(e^{j\omega}) = \sum_{n=-\infty}^{\infty} x[n] e^{-j\omega n}$

S: $x[n] = \frac{1}{2\pi} \int_{-\pi}^{\pi} X(e^{j\omega}) e^{j\omega n} d\omega$

* Discrete Time Signal

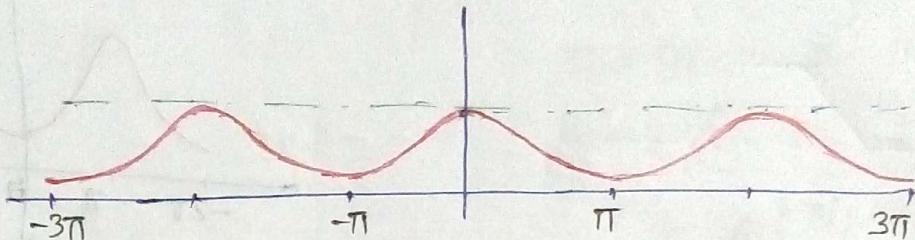is periodic with 2π period in frequency domain : $X(e^{j(\omega+2m\pi)}) = X(e^{j\omega})$



① $x_i[n] \leftrightarrow X_i(e^{j\omega})$



$$\sum_{i=1}^P a_i x_i[n] \leftrightarrow \sum_{i=1}^P a_i X_i(e^{j\omega})$$

② $x[n] \leftrightarrow X(e^{j\omega})$



$$x[n-n_0] \leftrightarrow e^{-jn_0\omega} (X(e^{j\omega}))$$

Time Delay / Advance : Magnitude Spectrum Remains unchanged
(Actual spectrum changes)

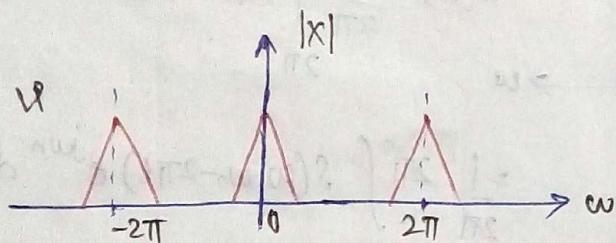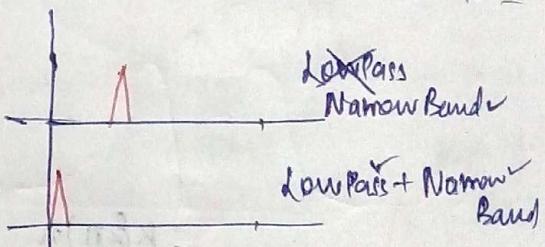③ $e^{j\omega n_0} x[n] \leftrightarrow X(e^{j(\omega+n_0)})$



(Narrow Band Low Pass)

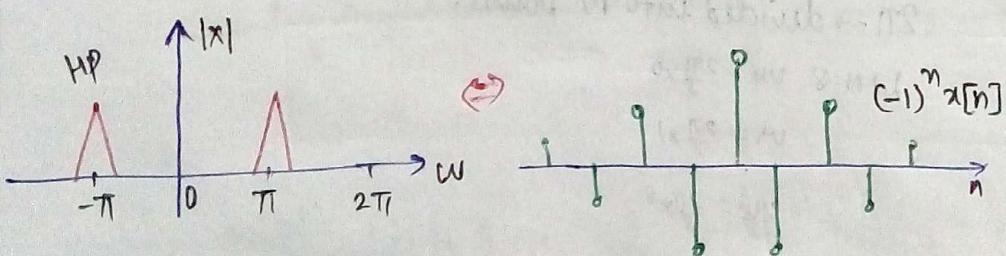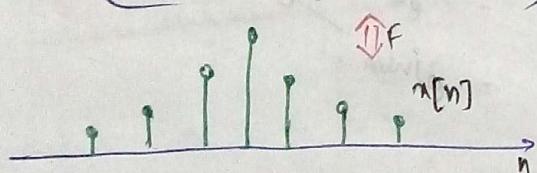


④ $x[n] \leftrightarrow X(e^{j\omega})$
 $x[-n] \leftrightarrow X(e^{-j\omega})$

$$(-1)^n x[n] \equiv e^{jn\omega} x[n] \quad (\text{with } \omega_0 = \pi) \\ \downarrow \\ X(e^{j(\omega-\pi)})$$

* Expansion in Time domain
↔ Compression in freq domain.

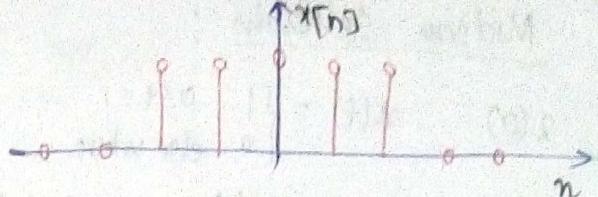* ⑤ $x_k[n] = \begin{cases} x[n/k], & \text{if } n = mk \\ 0, & \text{otherwise} \end{cases}$





$$X_{(k)}(e^{j\omega}) = \sum_{m=-\infty}^{\infty} x_{(k)}[m] e^{-j\omega mk}$$

$$= \sum_{m=-\infty}^{\infty} x[m] e^{-j(\omega k)m} = X(e^{jk\omega})$$

$$x_{(k)}[mk] = x\left[\frac{mk}{k}\right] = x[m]$$

- All signal processing is done in Time domain only.

LHS *(Real Operation)	RHS (For understanding implication of operation to be done)
$x[n]$	$X(e^{j\omega})$

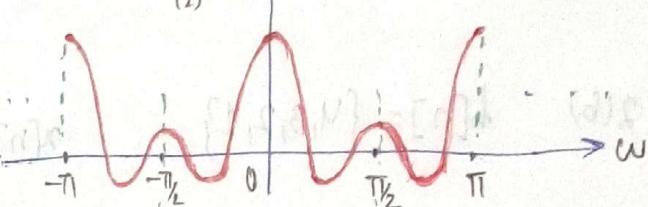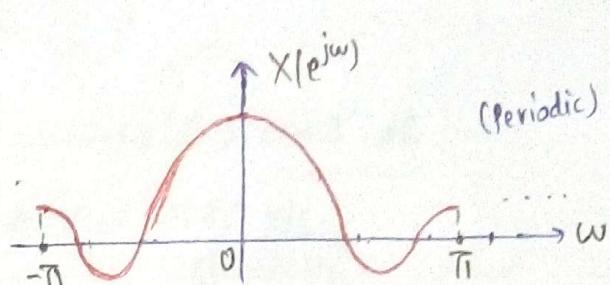

⑥ $x[n] \leftrightarrow X(e^{j\omega})$

$$\Rightarrow x[n] \leftrightarrow j \frac{d}{d\omega} X(e^{j\omega})$$

⑦ Parseval's Reln \rightarrow (Energy Spectral Density)

$$\sum_{n=-\infty}^{\infty} |x[n]|^2 = \frac{1}{2\pi} \int_{-\pi}^{\pi} |X(e^{j\omega})|^2 d\omega$$

⑧ $y[n] = h[n] * x[n]$
 $Y(e^{j\omega}) = H(e^{j\omega}) X(e^{j\omega})$

$$y[n] = x_1[n] x_2[n]$$

$$Y(e^{j\omega}) = \frac{1}{2\pi} \int_{-\pi}^{\pi} X_1(e^{j\theta}) X_2(e^{j(\omega-\theta)}) d\theta$$



* Read Group Delay in Opp.
(+ Pictures)

Midsem Solutions :

2(a) $x(t) = \begin{cases} 1 & 0 \leq t \leq 1 \\ 0 & \text{elsewhere} \end{cases}$

$$h(t) = \alpha(t/\alpha) \quad 0 < \alpha \leq 1$$

$$y(t) = x(t) * h(t)$$

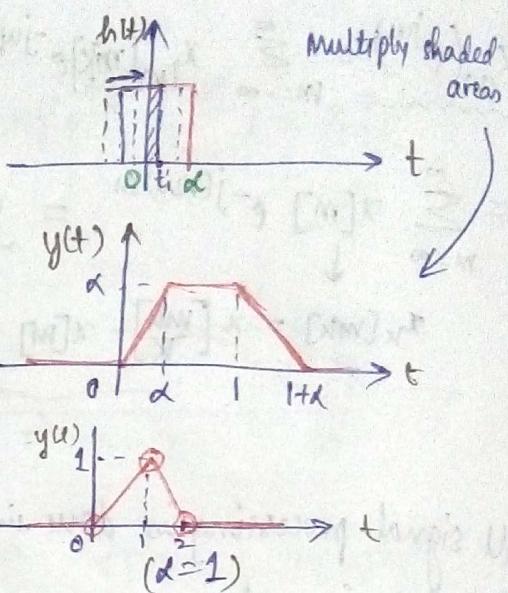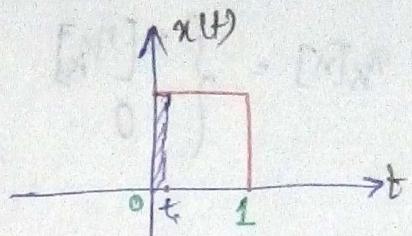


2(b) $h[n] = \{4, 3, 2, 1\}$

$$x[n] = \{-3, 7, 4\}$$


n	h	-3	7	4
4		-12	28	16
3		-9	21	12
2		-6	14	8
1		-3	7	4

$$y[n] = \{-12, 19, 31, 23, 15, 4\}$$

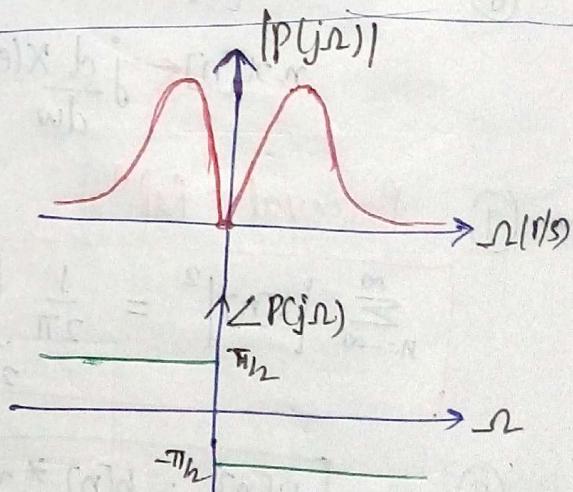
3(a) $P(j\omega) = \int_{-\infty}^{\infty} p(t) e^{-j\omega t} dt = \frac{-2j\omega}{\omega^2 + \alpha^2}$



3(b) $P(j\omega) = -\frac{2j}{\omega}$

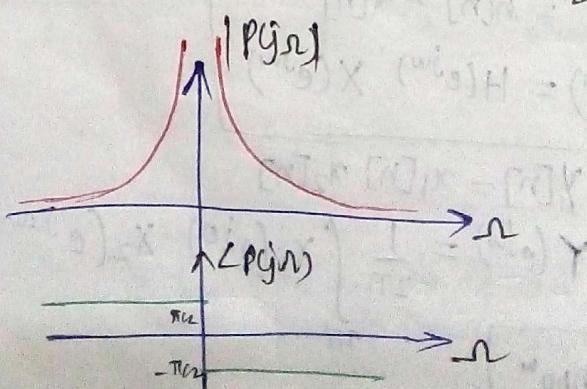

3(c)

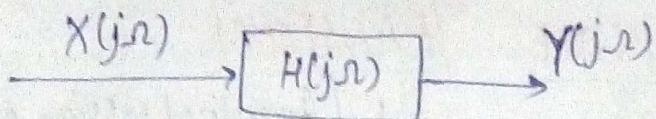

$$H(j\omega) = \frac{1}{j\omega + 1}$$

$\omega_c = 2\pi 80$

$$\angle H(j\omega) = -\tan^{-1}\left(\frac{\omega}{2\pi 80}\right)$$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + (\frac{\omega}{\omega_c})^2}}$$

$$20 \log |H(j\omega)| = -20 \log (\sqrt{2}) = -3 \text{ dB.}$$

$$\Rightarrow \omega = \omega_c = 2\pi 80 \text{ rad/s.}$$

$$f_i^{(1)} = 20 \text{ Hz}$$

$$f_i^{(2)} = 200 \text{ Hz.}$$

$$F_c = 80 \text{ Hz}$$

$$x(t) = 5 \cos(2\pi f_i t)$$

$$|H|_{20 \text{ Hz}} = \frac{1}{\sqrt{1 + (\frac{1}{4})^2}} = \frac{4}{\sqrt{17}}$$

$$\angle H = -\tan^{-1}(\frac{1}{4})$$

$$\% \text{ Mag.} = (\frac{A_p \text{ Mag}}{A_i \text{ Mag}}) \times \left(\text{Gain at } f_i = \frac{1}{20 \text{ Hz}} \right)$$

$$y(t) = 5 \times \frac{4}{\sqrt{17}} \cos\left(2\pi \times 20t - 0.245\right)$$

4(a).

1. Shift
2. Scale/Multiply.

4(c).

(i) No

(ii) Mathematically, $\frac{dy}{dt}$ is not causal (we can do forward diff' or backward diff')

But here, Yes.

(iii) Yes

(iv) Yes

For continuous time case

LAPLACE TRANSFORM

(Generalized version of Fourier Transform)

$$e^{st} \longrightarrow H(s) e^{st}$$

$$y(t) = \int_{-\infty}^{\infty} h(\tau) u(t-\tau) d\tau$$

$$= \int_{-\infty}^{\infty} h(\tau) e^{s(t-\tau)} d\tau$$

$$= e^{st} \int_{-\infty}^{\infty} h(\tau) e^{-s\tau} d\tau$$

$$= e^{st} H(s)$$

$$H(s) = \int_{-\infty}^{\infty} h(\tau) e^{-s\tau} d\tau$$

Analysis eqn

$$s = \sigma + j\omega$$

$$H(s) = \int_{-\infty}^{\infty} h(\tau) e^{-\sigma\tau} e^{-j\omega\tau} d\tau$$

$$\mathcal{L}(u(t)) \leftrightarrow F(u(t) e^{-\sigma t})$$

Laplace Transform

Fourier Transform

$$u(t) = e^{-at} u(t)$$

$$H(s) = \int_{-\infty}^{\infty} h(\tau) e^{-s\tau} d\tau$$

$$X(s) = ?$$

$$X(j\omega) = \int_{-\infty}^{\infty} (e^{-at} u(t) e^{-j\omega t}) dt = \int_0^{\infty} e^{-(a+j\omega)t} dt = \frac{1}{a+j\omega}, a > 0.$$

$$X(s) = X(\sigma + j\omega) = \frac{1}{(\sigma + a) + j\omega}, \sigma + a > 0, \sigma > -a$$

Region of Convergence

$$e^{-at} u(t) \leftrightarrow \frac{1}{s+a}, \operatorname{Re}\{s\} > -a$$


$$u(t) = -e^{-at} u(t)$$

$$X(s) = \int_{-\infty}^{\infty} u(t) e^{-st} dt$$

$$= - \int_{-\infty}^0 e^{-at} e^{-st} dt = \frac{e^{-(a+s)t}}{a+s} \Big|_{-\infty}^0$$


$$= \frac{1 - e^{-(a+s)(-\infty)}}{a+s} = \frac{1}{s+a}$$
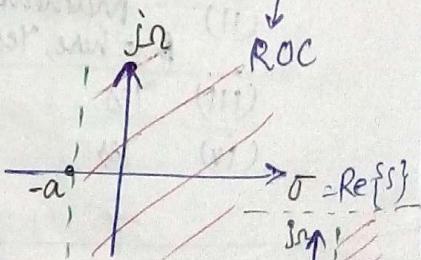
$$\operatorname{Re}\{s\} < -a \quad \text{ROC}$$



Laplace Transform - Mandatory to specify ROC.
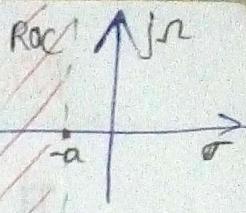
$$-e^{-at} u(-t) \leftrightarrow \frac{1}{s+a}, \text{ Re}\{s\} < -a$$



- L.T. can be computed only in ROC.

- If Imaginary axis is within ROC, then only F.T. exist.

- So, if $a < 0$, F.T. does not exist in previous case when $x(t) = e^{-at} u(t)$.


- F.T. is done on imaginary plane.

- ★** F.T. is Laplace transform evaluated on $j\omega$ axis.

$$x(t) = k_1 e^{at} u(t) + k_2 e^{-bt} u(t) \\ = x_1(t) + x_2(t)$$

$$X_1(s) = \frac{k_1}{s+a}, \text{ ROC: } \text{Re}\{s\} > -a$$
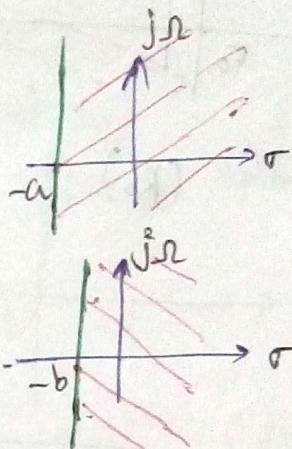
$$X_2(s) = \frac{k_2}{s+b}, \text{ ROC: } \text{Re}\{s\} > -b$$




$$X(s) = \frac{k_1(s+b) + k_2(s+a)}{(s+a)(s+b)}$$

$$X(s) = \frac{(k_1+k_2)\left[s + \frac{k_1b+k_2a}{k_1+k_2}\right]}{(s+a)(s+b)}, \text{ ROC: } \{x(s)\} > -b$$

$$= \frac{N(s)}{D(s)} \quad D(s): s = -a, s = -b \rightarrow \text{Poles} \quad \times$$

$$N(s): s = -\left(\frac{k_1b+k_2a}{k_1+k_2}\right) \leftarrow \text{Zero} \quad \circ$$
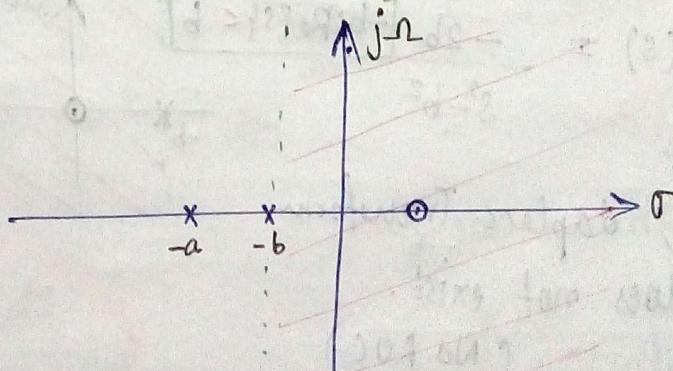
$$\begin{aligned} \text{Let } k_1 = 3, k_2 = -2 \\ a = 2, b = 1 \end{aligned}$$



* Pole location is excluded from ROC.

* $u(t) \rightarrow$ finite duration, absolutely integrable
 \downarrow
 ROC = Entire Region.



Equal Roots: $s = a, s = a$ \times (Double Cross)
 2nd order

Pull-zero plot.

ROC in Laplace Transform




03/10/16

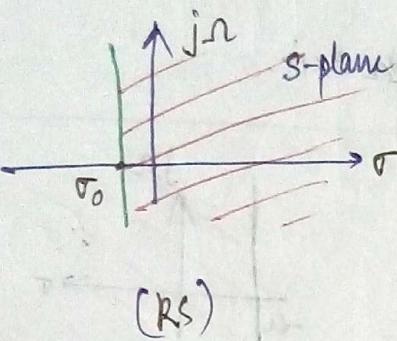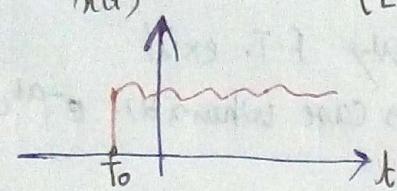If $x(t)$ is RS, if $\operatorname{Re}\{s\} = \sigma_0$ is in ROC
 (Right sided) (LS)



then $\forall s$, for which

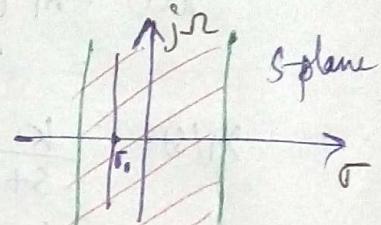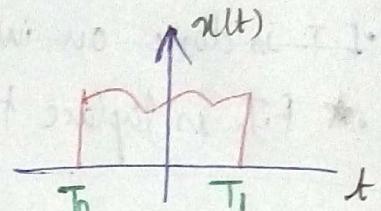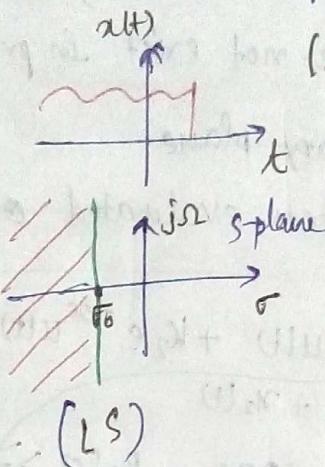$\operatorname{Re}\{s\} > \sigma_0$ will be in ROC.
 $(\operatorname{Re}\{s\} < \sigma_0)$




A strip contains σ_0 \leftarrow (2 sided)

$$x(t) = e^{-bt} u(t) \\ = e^{-bt} u(t) + e^{bt} u(-t)$$

$$e^{-bt} u(t) \xleftrightarrow{\mathcal{L}} \frac{1}{s+b}$$



$$e^{bt} u(-t) \xleftrightarrow{\mathcal{L}} \frac{-1}{s-b}$$
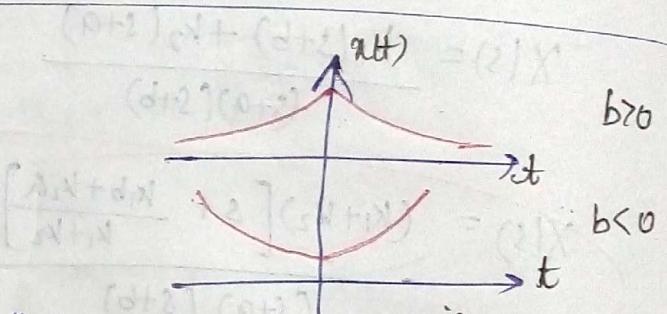
$$X(s) = \frac{-2b}{s^2 - b^2} \quad [-b < \operatorname{Re}\{s\} < b]$$



$$\operatorname{Re}\{s\} > -b$$

$$\operatorname{Re}\{s\} < b$$

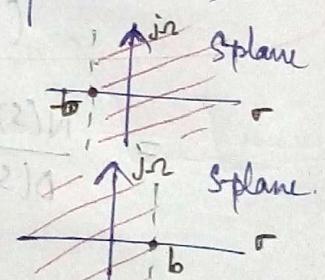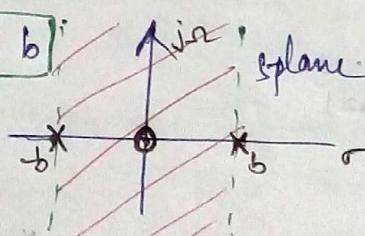

If $b \leq 0$, Laplace Transform
does not exist.

(No ROC)

Laplace Transform exists only for $b > 0$.

Here, ROC is bounded
by poles.

* If $x(t)$ is exponential $\Rightarrow X(s)$ is rational.

* Inside ROC, there should not be any poles.


* If $X(s)$ rational

→ If $x(t) \in \text{RS}$


↳ ROC will be right of right most pole

→ If $x(t) \in \text{LS} \rightarrow \dots$

$$X(s) = \frac{1}{(s+1)(s+3)}$$

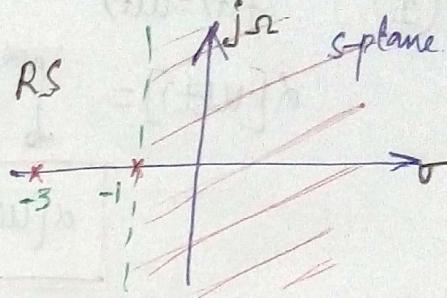


Anti-causal

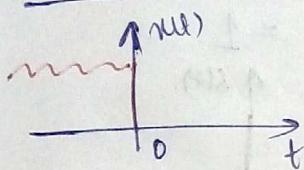


for $t > 0, x(t) = 0 \Rightarrow \text{LS}$
 $t < 0, x(t) = \text{finite}$

Causal

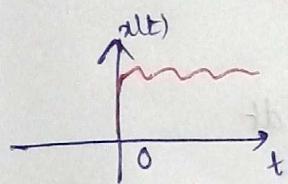

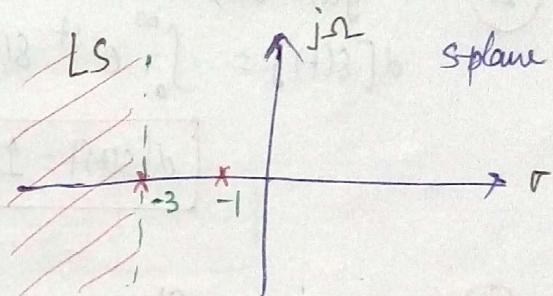for $t < 0, x(t) = 0 \Rightarrow \text{RS}$
 $t > 0, x(t) = \text{finite}$



* $\mathcal{F}\{x(t)\} = \mathcal{L}\{x(t)\}_{\sigma=0}$


* $X(\sigma+j\omega) = \mathcal{F}\{x(t)e^{-\sigma t}\} = \int_{t=-\infty}^{\infty} \{x(t)e^{-\sigma t}\} e^{-j\omega t} dt$

→ $x(t)e^{-\sigma t} = \mathcal{F}^{-1}\{X(\sigma+j\omega)\} = \frac{1}{2\pi} \int_{\sigma-j\infty}^{\sigma+j\infty} X(\sigma+j\omega) e^{j\omega t} d\omega$

⇒ $x(t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} X(\sigma+j\omega) e^{(\sigma+j\omega)t} d\omega$

⇒ $x(t) = \frac{1}{2\pi j} \int_{\sigma-j\infty}^{\sigma+j\infty} X(s) e^{\sigma t} ds$

$s = \sigma + j\omega$
 $ds = jd\omega$

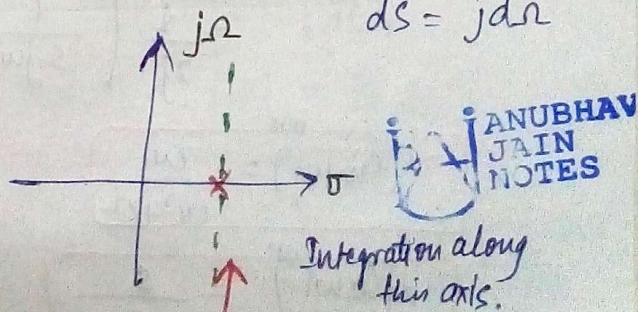

Integration along this axis.

Circuit Analysis in s-domain

One Sided L.T.


$$s = \sigma + j\omega$$

$$\mathcal{L}[f(t)] = \int_0^\infty e^{-st} f(t) dt = F(s)$$

1

$$f(t) = u(t)$$
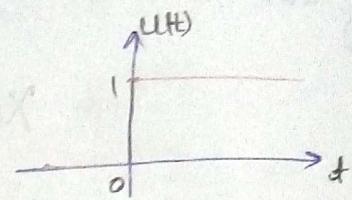
$$\mathcal{L}[u(t)] = \int_0^\infty e^{-st} u(t) dt = \left[\frac{e^{-st}}{-s} \right]_0^\infty$$




$$\mathcal{L}[u(t)] = \frac{1}{s}$$

2

$$f(t) = \delta(t)$$

$$\mathcal{L}[\delta(t)] = \int_0^\infty e^{-st} \delta(t) dt = \int_0^0 e^{-st} \delta(t) dt = 1$$

$$\mathcal{L}[\delta(t)] = 1$$

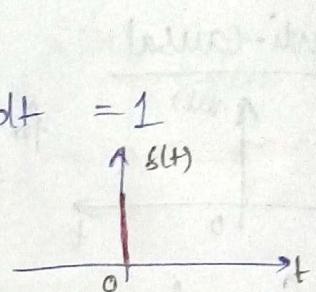

3

$$f(t) = e^{at} u(t)$$


$$\mathcal{L}[e^{at} u(t)] = \int_0^\infty e^{-st} e^{at} u(t) dt = \int_0^\infty e^{-(s-a)t} dt$$

$$\mathcal{L}[e^{at} u(t)] = \frac{1}{s-a}$$

4

$$\mathcal{L}[\sin wt] \quad \& \quad \mathcal{L}[\cos wt]$$
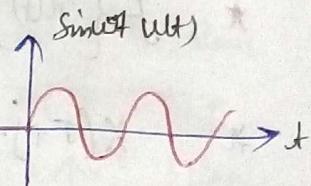
$$\hookrightarrow \int_0^\infty e^{-st} \sin wt u(t) dt$$



$$\sin wt = \frac{e^{j\omega t} - e^{-j\omega t}}{2j}$$

$$\mathcal{L}[\sin wt] = \frac{1}{2j} \int_0^\infty [e^{-(s-j\omega)t} - e^{-(s+j\omega)t}] u(t) dt$$

$$= \frac{1}{2j} \left[\frac{1}{s-j\omega} - \frac{1}{s+j\omega} \right] = \frac{s+j\omega - s+j\omega}{2j(s^2+\omega^2)}$$

$$\mathcal{L}[\sin wt] = \frac{\omega}{s^2 + \omega^2}$$

$$\mathcal{L}[\cos wt] = \frac{s}{s^2 + \omega^2}$$

$$\alpha \left[\frac{df}{dt} \right] = ?$$

$$d[f(t)] = f(s)$$

(5)

$$F(s) = \int_0^\infty e^{-st} f(t) dt$$

$$\frac{df}{ds} = \int_0^\infty \frac{d}{ds} (e^{-st}) f(t) dt$$

$$= \int_0^\infty (-t) e^{-st} f(t) dt$$

$$\frac{df}{ds} = - \int_0^\infty e^{-st} (t \cdot f(t)) dt$$

$$-\frac{df}{ds} = d[t \cdot f(t)]$$

$$\boxed{\alpha [t \cdot f(t)] = -\frac{df}{ds}}$$

$$\& \boxed{\alpha [f(t)] = F(s)}$$

(6)

$$\alpha \left[\frac{df}{dt} \right] = \int_0^\infty e^{-st} \frac{df}{dt} u(t) dt$$

$$= \int_0^\infty e^{-st} \frac{df}{dt} dt = \left[e^{-st} f \right]_0^\infty - \int_0^\infty (-s)e^{-st} f(t) dt$$

$$= -f(0) + s \int_0^\infty e^{-st} f(t) dt$$

$$\boxed{\alpha \left[\frac{df}{dt} \right] = -s F(s) - f(0)}$$

(7)

$$\alpha \left[\frac{d^2 f}{dt^2} \right] = \alpha \left[\frac{d}{dt} \left(\frac{df}{dt} \right) \right] = s \left[s F(s) - f(0) \right] - \left(\frac{df}{dt} \right)_0$$

$$= \boxed{s^2 F(s) - s f(0) - \frac{df}{dt}(0)}$$


$$\rightarrow \alpha \left[\int_0^t f(z) dz \right] = ?$$

$$8 \quad \text{Let } \int_0^t f(z) dz = g(t) \quad \therefore \frac{dg}{dt} = f(t).$$

$$\int_0^\infty e^{-st} g(t) dt = \left[g(t) \left(\frac{e^{-st}}{-s} \right)_0^\infty - \int_0^\infty \frac{dg}{dt} \left(\frac{e^{-st}}{-s} \right) dt \right] \\ = \frac{g(0)}{s} + \frac{1}{s} \int_0^\infty f(t) e^{-st} dt$$

$\mathcal{L} \left[\int_0^t f(z) dz \right] = \frac{g(0)}{s} + \frac{F(s)}{s}$

$$\mathcal{L}^{-1} \left(\frac{C}{s^2 + \omega^2} \right) = \sin \omega t U(t)$$

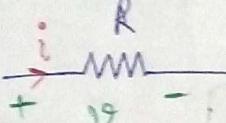
* 

$$i = \frac{v}{R} \quad (\text{time domain})$$

$$I(s) = \frac{V(s)}{R} \quad (\text{s domain})$$

or $\boxed{V(s) = RI(s)}$




{ Capital letters = Transformed }

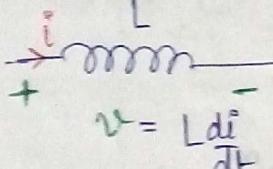* 

$$V(s) = L \left[sI(s) - i(0) \right]$$

if $i(0) = 0$

$\boxed{V(s) = Ls I(s)}$

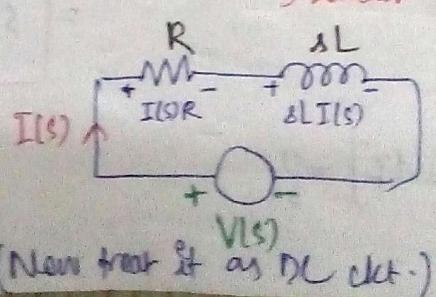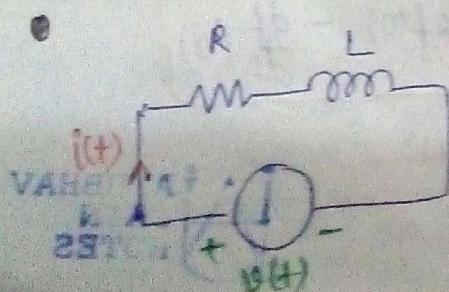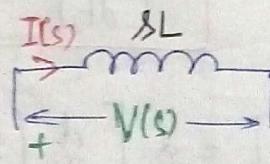


$$V(s) = RI(s) + SL I(s)$$

$$V(s) = (R+SL) I(s)$$

$$I(s) = \frac{V(s)}{R+SL}$$

$$I(s) = \frac{E/s}{R+SL}$$

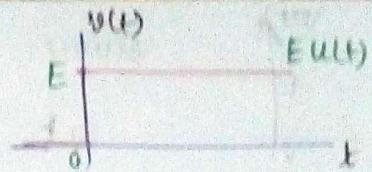

$$V(t) = E u(t)$$


$$I(s) = \frac{E/L}{s(s+R_L)}$$

$$\therefore V(s) = \frac{E}{s}$$

$$= \frac{E}{L} \left[\frac{1/R}{s} - \frac{1/R}{s+R_L} \right]$$




$$I(s) = \frac{E}{R} \left[\frac{1}{s} - \frac{1}{s+R_L} \right]$$
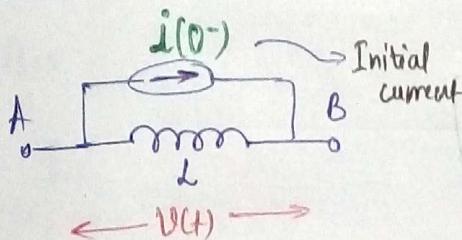
$$i(t) = \frac{E}{R} [1 - e^{-R_L t}] u(t)$$




Initially charge inductor

\equiv (Initially uncharged) || (current source)

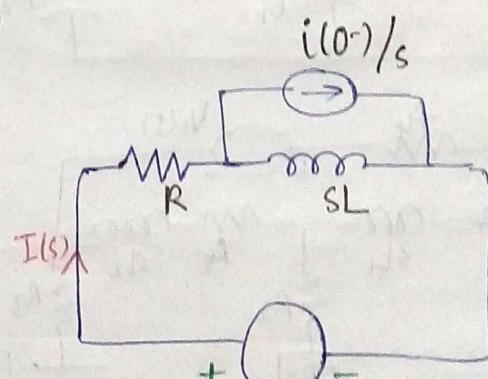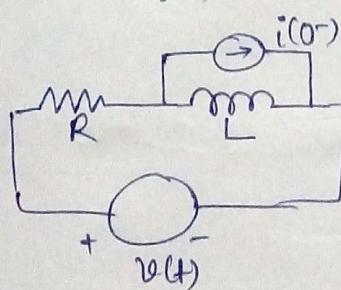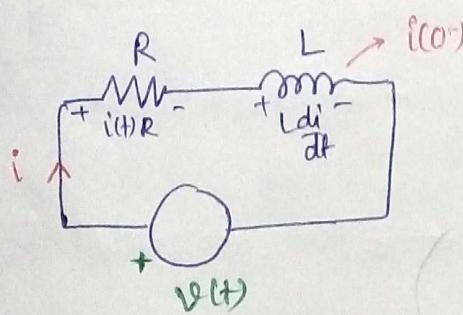



Apply Superposition.

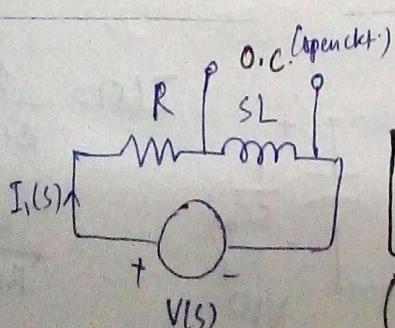

$$I_1(s) = \frac{V(s)}{R+sL}$$
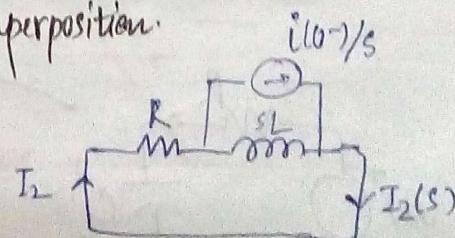
$$I_2(s) = \frac{i(0-)}{s} \frac{sL}{R+sL}$$



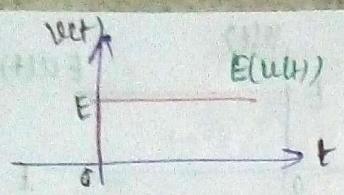


$$\bullet \quad \alpha^{-1} \left\{ \frac{V(s)}{R+SL} \right\} = \frac{E}{R} (1 - e^{-R_L t})$$

$$\bullet \quad \alpha^{-1} \left\{ i(0^+) \frac{sL}{R+SL} \right\} = i(0^+) \alpha^{-1} \left\{ \frac{1}{s+R_L} \right\} = i(0^+) e^{-R_L t}$$

$$i(t) = \frac{E}{R} (1 - e^{-R_L t}) + i(0^+) e^{-R_L t}$$

*

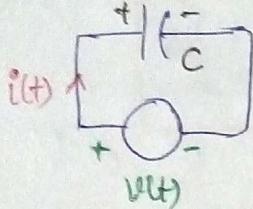




$$c \frac{du}{dt} = i$$

$$v(t) = \frac{1}{c} \int_0^t i dt = v(0^+) + \frac{1}{c} \int_0^t i dt$$

$$V(s) = \frac{v(0^+)}{s} + \frac{I(s)}{sc}$$

if $v(0^+) = 0$

$$V(s) = \frac{1}{sc} I(s)$$

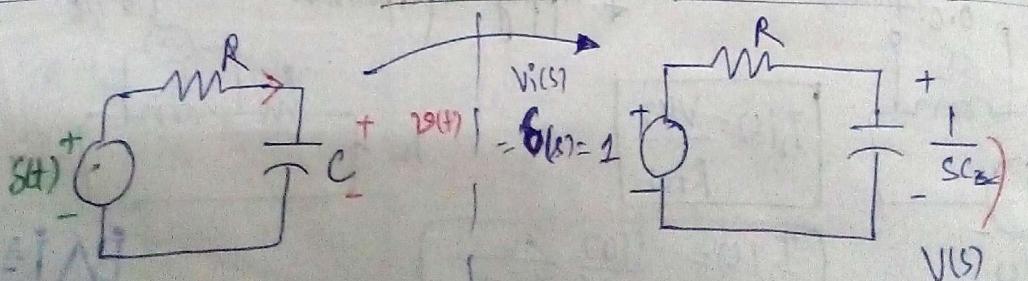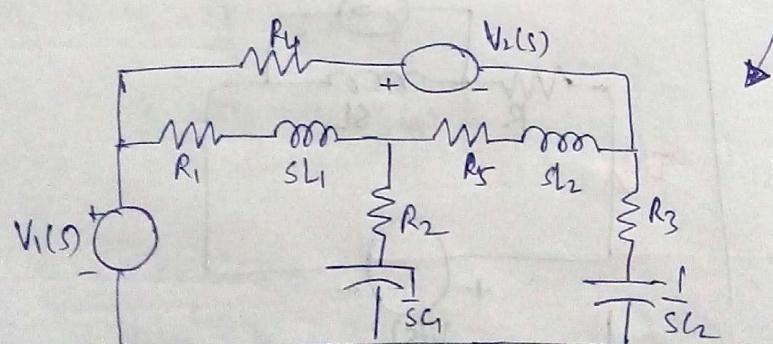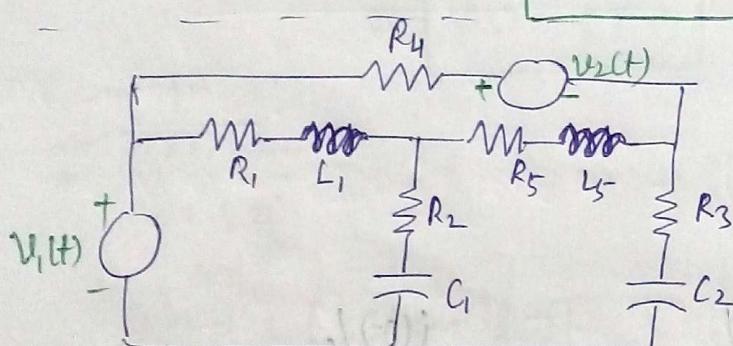


$$I(s) = \frac{1 - V(s)}{R + \frac{1}{sc}}$$

$$= \frac{sc}{Rsc + 1}$$


$$V(s) = I(s) \frac{1}{sC} = \frac{1}{1+RCS} = \frac{1}{RC} \left(\frac{s+1}{s+1/RC} \right)$$

$$v(t) = \frac{1}{RC} e^{-t/RC}$$

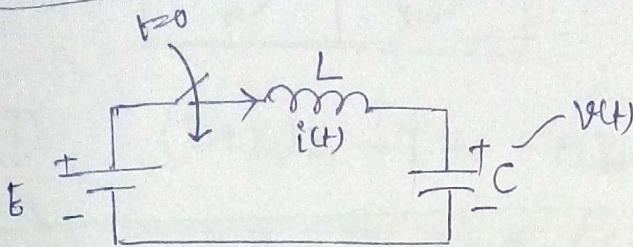

$$\omega^2 = \frac{1}{LC}$$
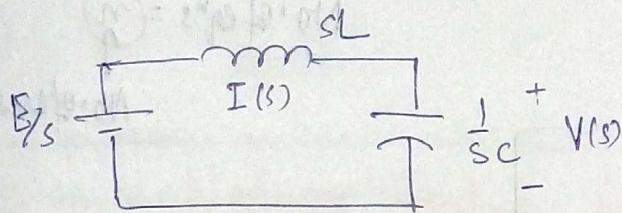
$$\frac{E}{s} = I(s) \left\{ sL + \frac{1}{sC} \right\}$$



$$I(s) = \frac{E/s}{sL + \frac{1}{sC}} = \frac{E}{s^2L + \frac{1}{C}}$$

$$= \frac{E/L}{(s-j\omega)(s+j\omega)}$$

$$V(s) = \frac{1}{sC} I(s)$$

$$= \frac{E}{LC} \frac{1}{s(s-j\omega)(s+j\omega)}$$

$$= \frac{E}{LC} \frac{1}{s^2 + \omega^2}$$

$$= \frac{E}{LC} \left(\frac{1}{s} - \frac{j\omega}{s^2 + \omega^2} \right) \frac{1}{\omega^2}$$

$$v(t) = E(u(t) - \cos \omega t u(t))$$

$$v(t) = E(1 - \cos \omega t) u(t)$$

$$I(s) = \frac{E}{L} \left\{ \frac{1}{s-j\omega} - \frac{1}{s+j\omega} \right\} \left(\frac{1}{2j\omega} \right)$$


$$i(t) = \frac{E}{2L\omega} (e^{j\omega t} - e^{-j\omega t}) u(t)$$

$$i(t) = \frac{E}{L\omega} \sin \omega t u(t)$$


$$v(t) = E - L \frac{di}{dt}$$

$$= E - L \left(\frac{E}{L\omega} \right) \omega \cos \omega t u(t)$$

$$v(t) = E(1 - \cos \omega t) u(t)$$

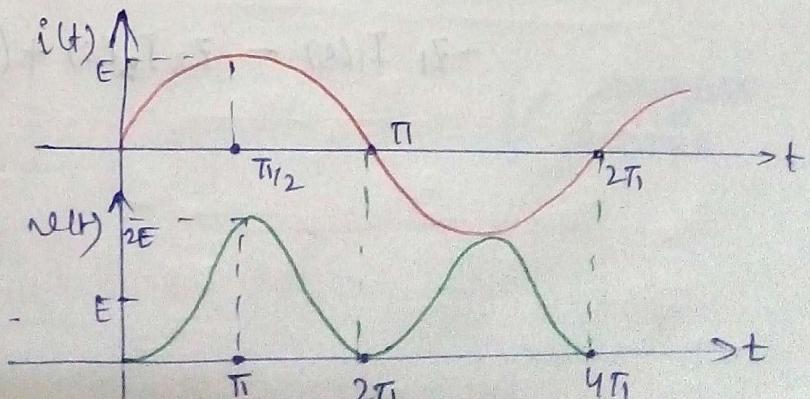

BANGLA
MAIN
NOTES

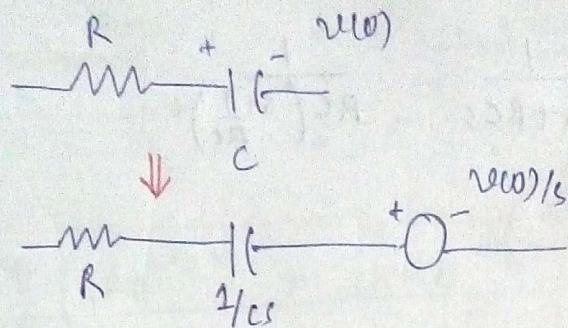


$$Z(s) = R + sL + \frac{1}{sC}$$

Mesh Analysis

No. of eqns = n

No. of Mesh.

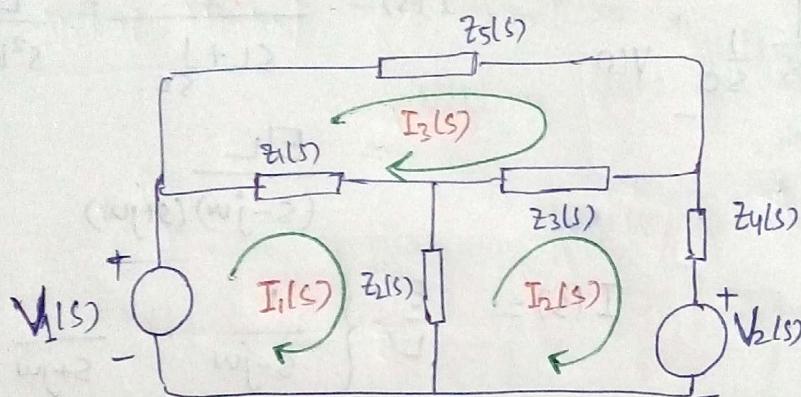

KVL in mesh ①:

$$V_1(s) - (I_1(s) - I_3(s))Z_1(s) - (I_1(s) - I_2(s))Z_2(s) = 0$$


$$(Z_1(s) + Z_2(s))I_1(s) - Z_2(s)I_2(s) - Z_1(s)I_3(s) = V_1(s)$$

KVL in mesh ②:

$$-Z_2 I_1(s) + (Z_2 + Z_3 + Z_4) I_2(s) - Z_3 I_3(s) = -V_2(s)$$

KVL in mesh ③:
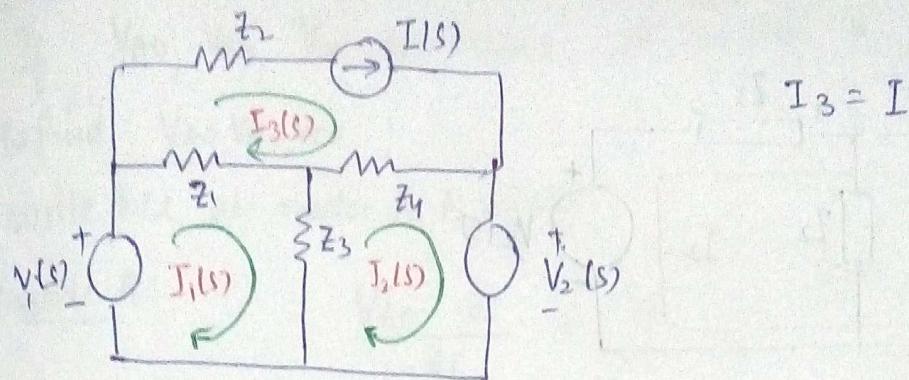
$$-Z_1 I_1(s) - Z_2 I_2(s) + (Z_1 + Z_3 + Z_5) I_3(s) = 0$$



$$\textcircled{1}: (Z_1 + Z_3)I_1 - IZ_1 - Z_3I_2 = V_1(s)$$

$$\textcircled{2}: -Z_3I_1 + (Z_3 + Z_4)I_2 - Z_4I = -V_2(s)$$



$$\textcircled{3}: I_3 = I.$$

Network Analysis in s-domain

06/10/16

$$Z(s) = R + sL + \frac{1}{sC}$$

$$V(s) = Z(s) I(s)$$

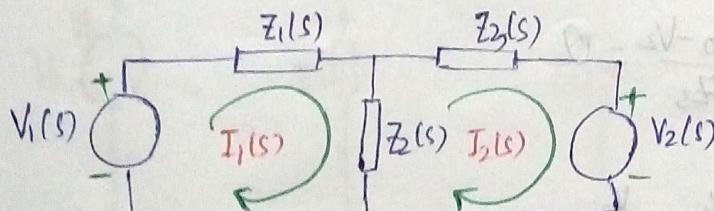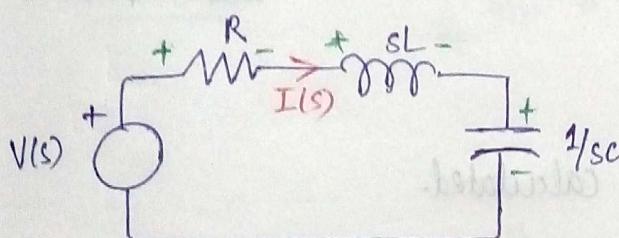

Mesh: in sdomain

$$\text{Mesh 1: } (Z_1 + Z_2)I_1 - Z_2I_2 = V_1$$

$$\text{Mesh 2: } -Z_2I_1 + (Z_3 + Z_2)I_2 = -V_2$$


$$\begin{bmatrix} Z_1 + Z_2 & -Z_2 \\ -Z_2 & Z_2 + Z_3 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ -V_2 \end{bmatrix}$$

B.A.I
ANUPRAV
IN NOTES

$$I_1(s) = \frac{\begin{vmatrix} V_1 & -Z_2 \\ -V_2 & Z_2 + Z_3 \end{vmatrix}}{|Z|}$$

(Cramer's Rule)

$$I_2(s) = \frac{\begin{vmatrix} Z_1 + Z_2 & V_1 \\ -Z_2 & -V_2 \end{vmatrix}}{|Z|}$$

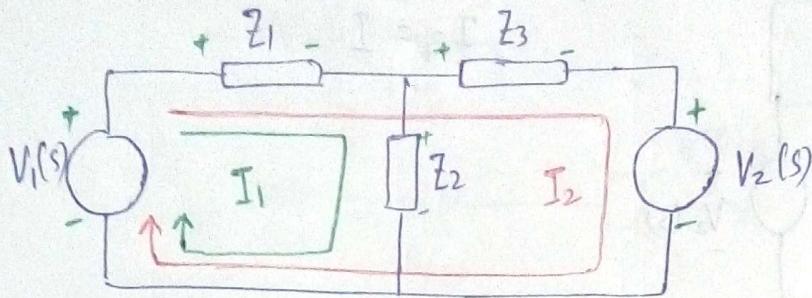


$$1: (Z_1 + Z_2) I_1 + Z_1 I_2 = +V_1$$

$$2: \cancel{Z_2 I_1} + Z_1 I_1 + (Z_1 + Z_3) I_2 = V_1 - V_2$$

Nodal Method

(s -domain)

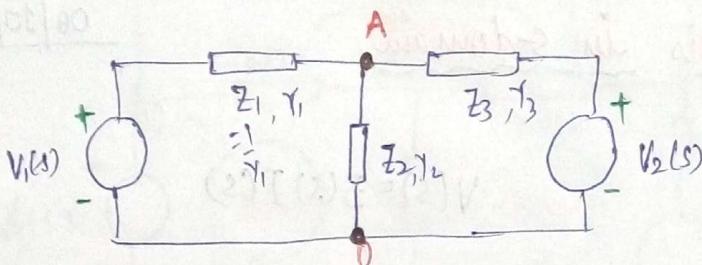Node: Junction where more than 2 elements are joined.



* No. of eq's = $m-1$

Total no. of nodes.

If V_{AO} is known,
all the currents can be calculated.


At node A write KCL

$$\frac{V_{AO}-V_1}{Z_1} + \frac{V_{AO}}{Z_2} + \frac{V_{AO}-V_2}{Z_3} = 0$$

$$\left(\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} \right) V_{AO} = \frac{V_1}{Z_1} + \frac{V_2}{Z_3}$$

$$(Y_1 + Y_2 + Y_3) V_{AO} = V_1 Y_1 + V_2 Y_3$$

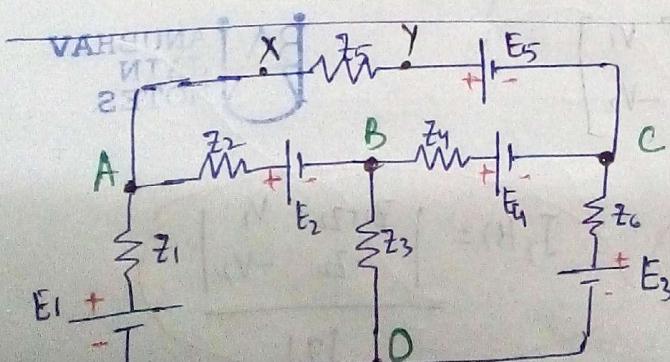$Z^{-1} = Y$
 $(\text{Impedance})^{-1} = \text{Admittance}$



$$\frac{\vec{V}_{xy}}{Z_5} = \frac{V_{x0} - V_{y0}}{Z_5} = \frac{V_{AO} - (V_{CO} + E_5)}{Z_5}$$

$$\frac{\vec{V}_{xy}}{Z_5} = \frac{V_{AO} - V_{CO} - E_5}{Z_5}$$

If V_{AO} , V_{BO} , V_{CO} are known, all currents can be calculated.

To find V_{AO}, V_{BO}, V_{CO} :

Write KCL at nodes A, B and C.

at node A:

$$\frac{V_{AO} - E_1}{Z_1} + \frac{V_{AO} - E_2 - V_{BO}}{Z_2} + \frac{V_{AO} - E_5 - V_{CO}}{Z_5} = 0$$

$$\left(\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_5} \right) V_{AO} - \frac{1}{Z_2} V_{BO} - \frac{1}{Z_5} V_{CO} = \frac{E_1}{Z_1} + \frac{E_2}{Z_2} + \frac{E_5}{Z_5}$$

Coefficients

Sum of all admittance connected
at node A.


negative of
sum of all
admittance
between nodes A & B

at Node B:

$$-\frac{1}{Z_2} V_{AO} + \left(\frac{1}{Z_2} + \frac{1}{Z_3} + \frac{1}{Z_4} \right) V_{BO} - \frac{1}{Z_4} V_{CO} = -\frac{E_2}{Z_2} + \frac{E_4}{Z_4}$$

at node C:
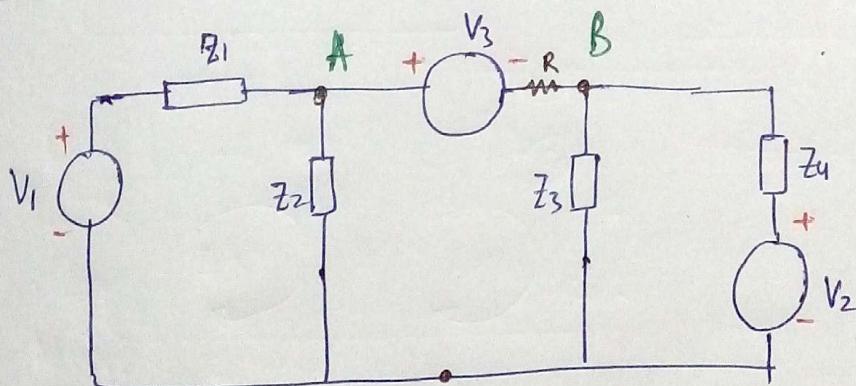
$$-\frac{1}{Z_5} V_{AO} - \frac{1}{Z_4} V_{BO} + \left(\frac{1}{Z_5} + \frac{1}{Z_4} + \frac{1}{Z_6} \right) V_{CO} = -\frac{E_5}{Z_5} - \frac{E_4}{Z_4} + \frac{E_3}{Z_6}$$



Nodal Analysis

$$A: \left(\frac{1}{Z_1} + \frac{1}{Z_2} + \left(\frac{1}{0} \right) \right) V_{AO} \times$$


Method 1 \Rightarrow Assume impedance between A & B $\rightarrow R$. } Solve completely & put $R=0$.

Method 2 \rightarrow choose 'B' as reference. (Change Ref.)

Method 3 \rightarrow (See next page)

Draw equivalent ckt diagram (assuming ideal voltage sources).

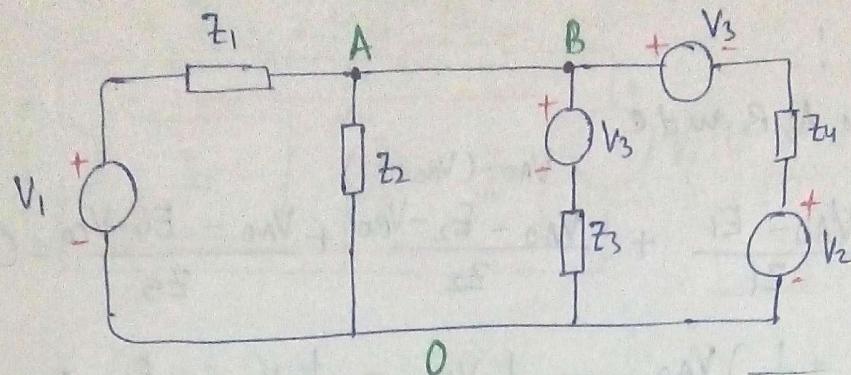\rightarrow Replace voltage source by short ckt & transfer it in subsequent branches.



17/10/16

* Steady State \rightarrow DC : $S=0$

Sinusoidal : $S=j\omega$


Here, we will get $\frac{1}{0}$ coefficients for V_{ab} , V_{bc}

Method 1: Assume some Z in ab branch.



After solving all equations,
put $Z=0$.

Method 2: Short Voltage Source E_4
& put in other connected branches.

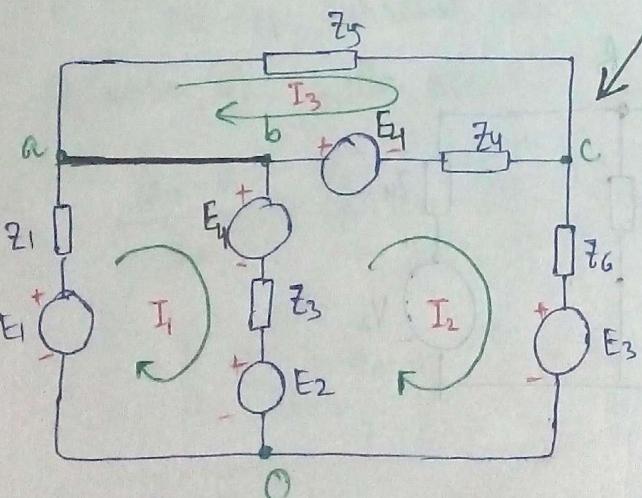Here, all loop (KVL) equations
are unchanged.




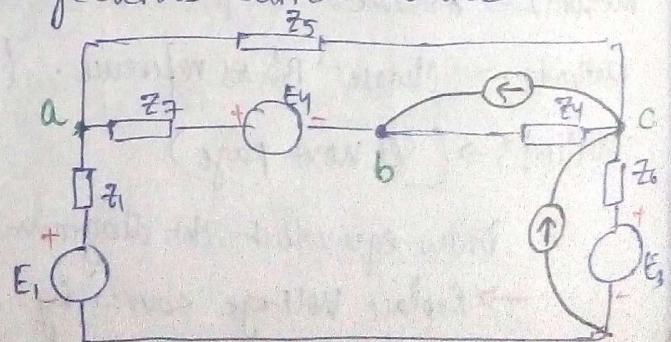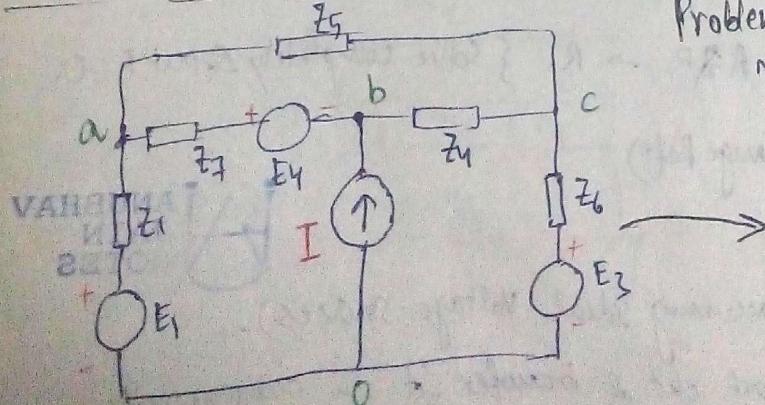Problem! In Mesh Analysis, we don't know
Voltage across current source.




Open Circuit Current Source
and transfer it to subsequent branches (parallel connection).


SUBSTITUTION TH.

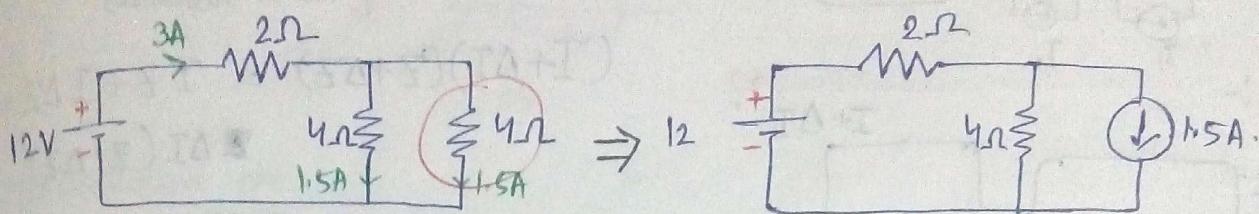

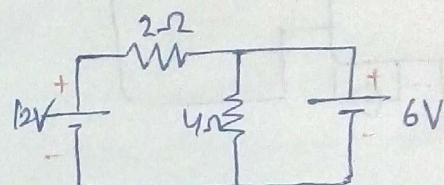
Identical dcts
(As long as current distribution is concerned)



* Proof of Thévenin's Th.

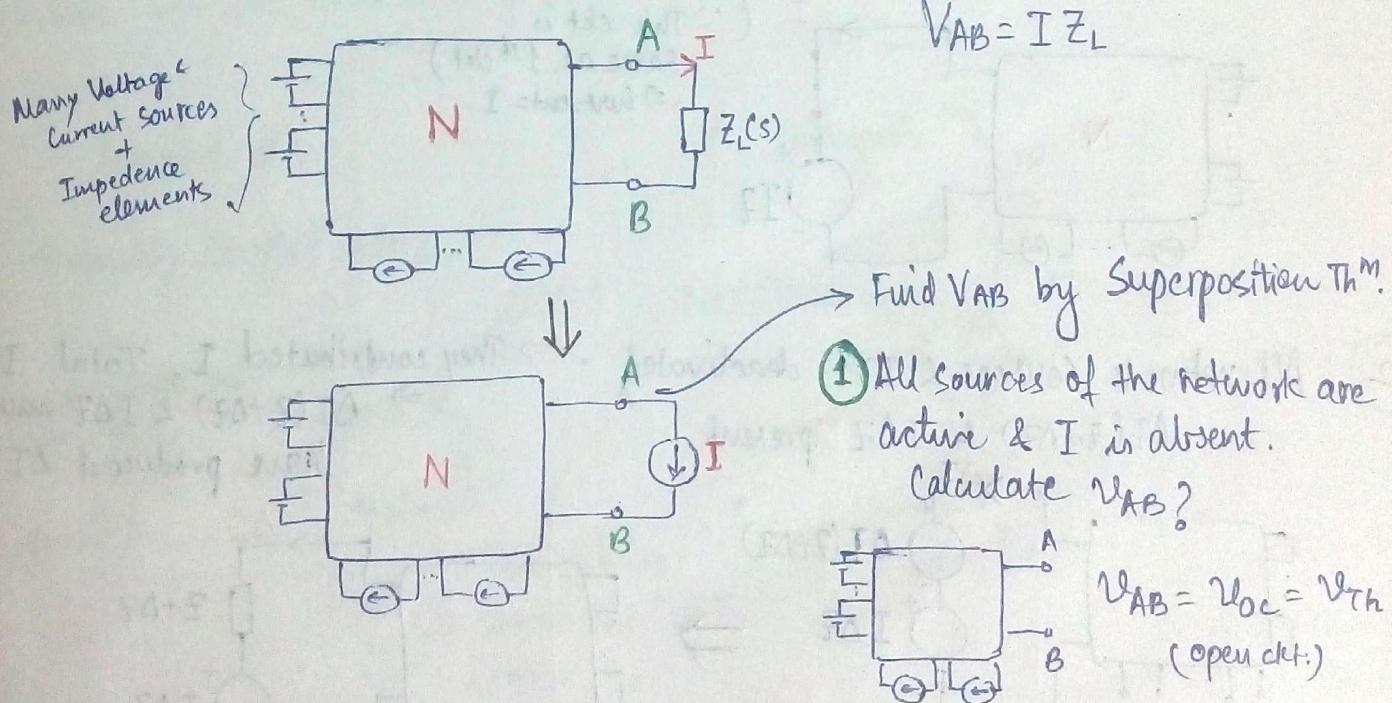


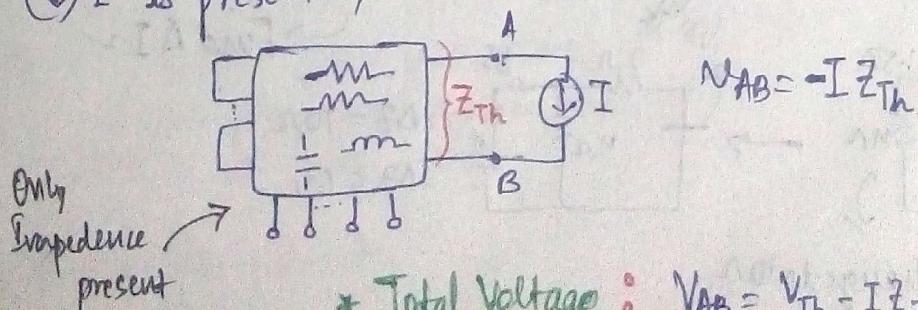- ② All sources of the network deactivated only
(1) I is present, calculate V_{AB} ?




$$* \text{Total Voltage : } V_{AB} = V_{Th} - I Z_{Th} = I Z_L \quad \left\{ I = \frac{V_{Th}}{Z_{Th} + Z_L} \right.$$

COMPENSATION Thm

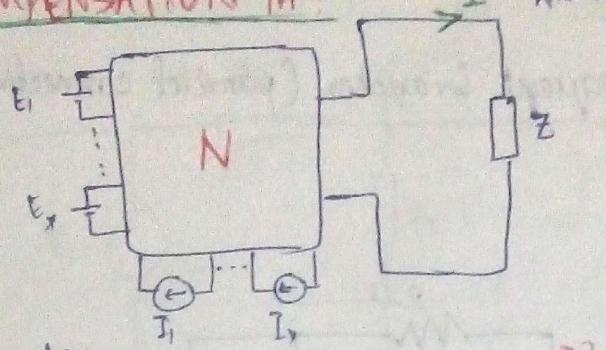


New ckt:-

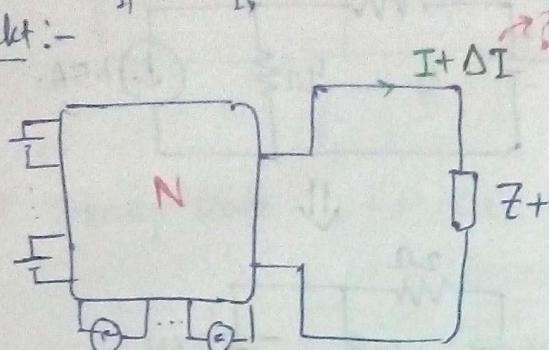


{ All in 'sdomain' }
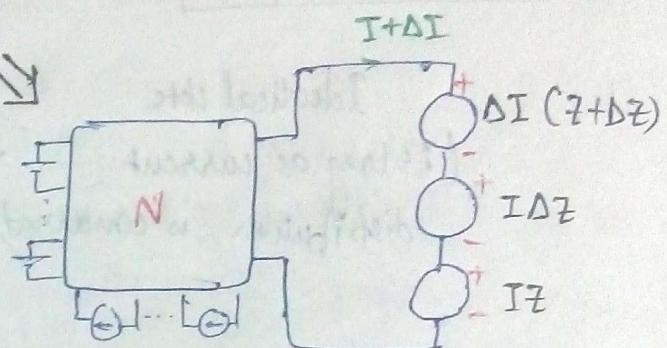
$$(I + \Delta I)(Z + \Delta Z) = IZ + I\Delta Z + \Delta I(Z + \Delta Z)$$




Apply Superposition Thm.

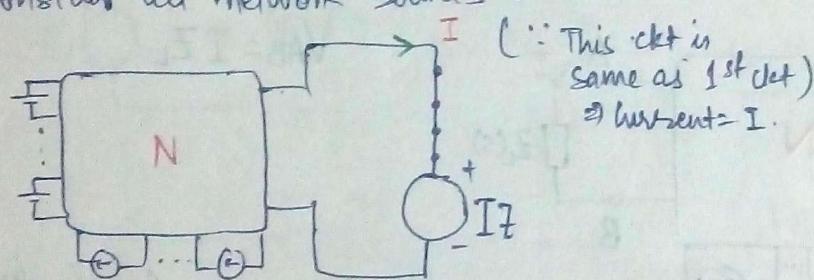
- ① Consider all network sources and IZ .




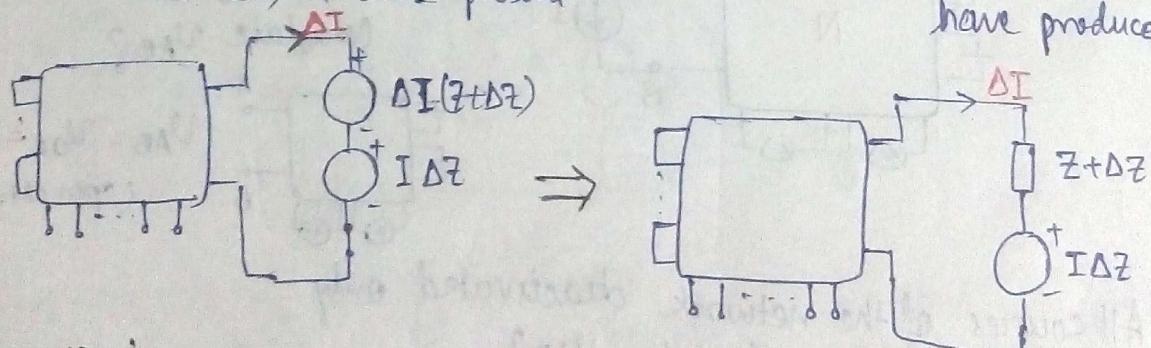
- ② All network sources & IZ deactivated, \rightarrow They contributed I , Total $I + \Delta I$
 $\Delta I(Z + \Delta Z)$ & $I\Delta Z$ present $\rightarrow \Delta I(Z + \Delta Z)$ & $I\Delta Z$ must have produced ΔI .



Application:-

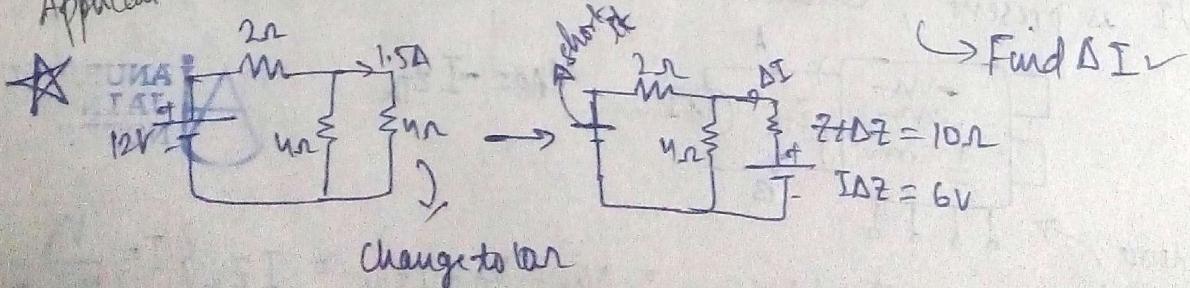


Change to var

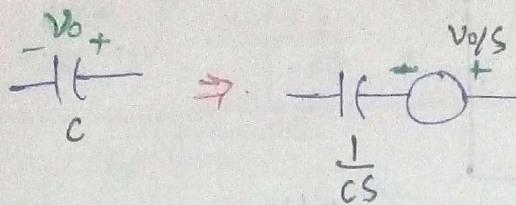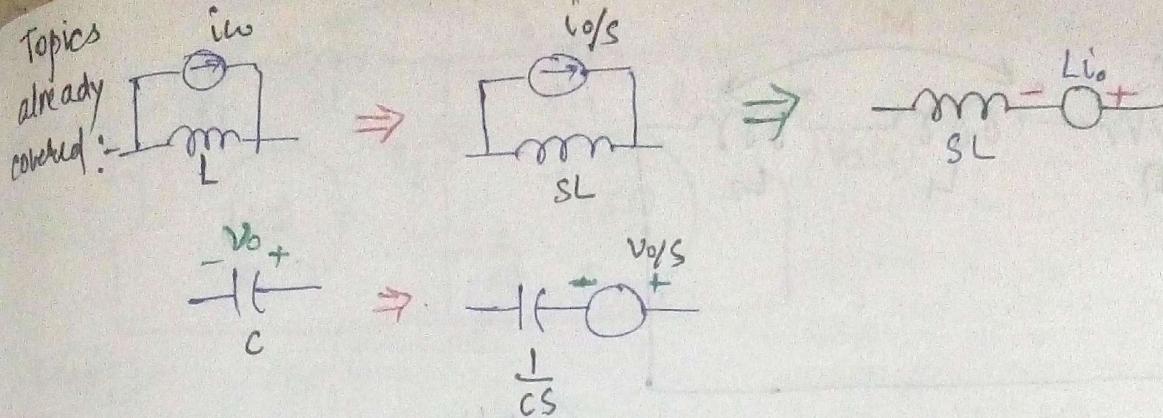

1. Transformed ckt.
 2. Mesh and Nodal Analysis
 3. Transferring voltage or current sources in unusual situations.
 4. Substitution Th. - its application.
 5. Compensation Th.
- * Key word: Laplace Transform and inverse L-T. for standard f's.


* Coupled ckt.

Mutually coupled coils

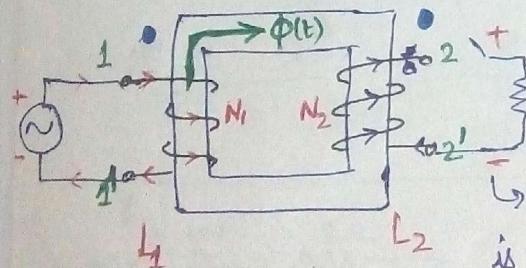

* Tellegen's Th.

Dot Convention

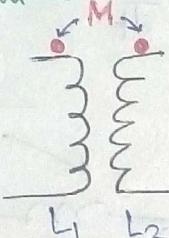


This polarity
is consistent with
Lenz's Law.

(Since flux produced opposes
the cause of induction $\rightarrow \Phi(t)$)

Dots \rightarrow Both sides will have
same polarity at a given time.
(Both + or both -)

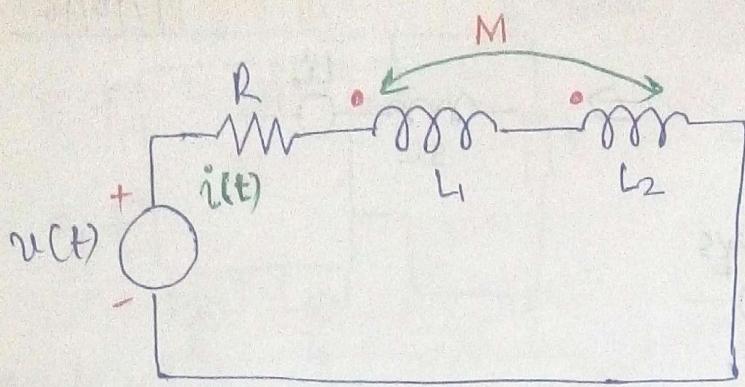\Rightarrow Dots represent like polarity.



$$v(t) = Ri + \left(L_1 \frac{di}{dt} \right) + \left(L_2 \frac{di}{dt} + M \frac{di}{dt} \right)$$

$\textcircled{+}$

due to L_2
due to L_1


$$V(s) = RI(s) + sL_1 I(s) + MSI(s) + sL_2 I(s) +$$

('+' here)

When current is entering L_2 , $\bullet_2 = +$


$$\Rightarrow \bullet_1 = +$$
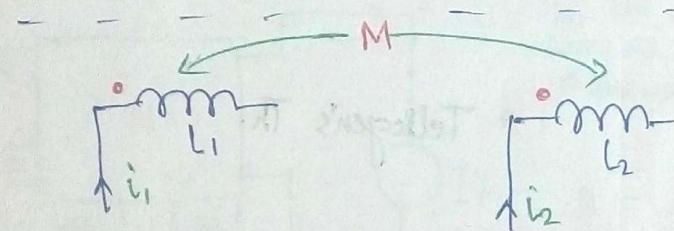
$$\Rightarrow \textcircled{+} M \frac{di}{dt} = + M \frac{di}{dt}$$




$$L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$
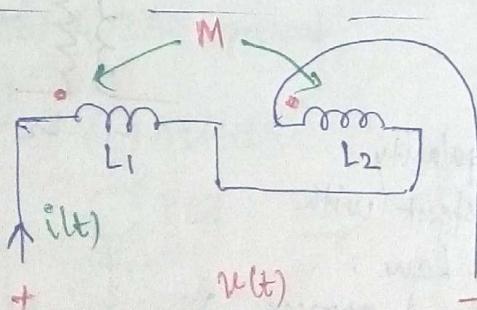
$$L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$



$$v(t) = \left(L_1 \frac{di}{dt} - M \frac{di}{dt} \right) + \left(L_2 \frac{di}{dt} - M \frac{di}{dt} \right)$$

14
15
16
17

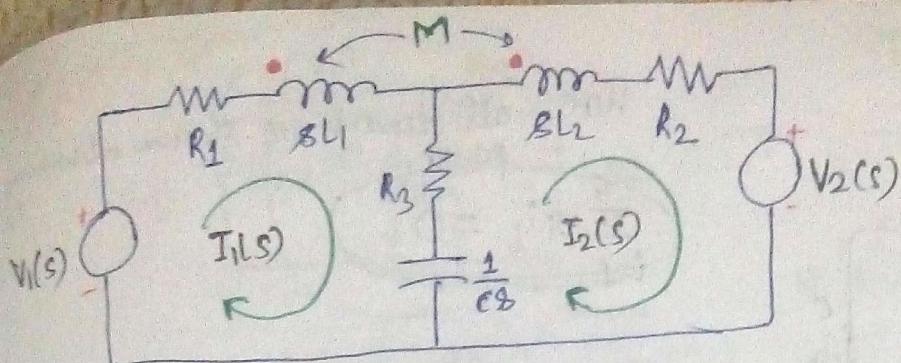

Mesh 1 :-

$$(R_1 + sL_1 + R_3 + \frac{1}{Cs}) I_1(s) = V_1(s) - MI_2(s)$$


$$\Leftrightarrow (R_3 + \frac{1}{Cs}) I_2(s)$$

Think in this way: Due to M , there will be additional voltage drop.


Assume it as a voltage source, write it with $V_{11}(s)$

Mesh 2 :-
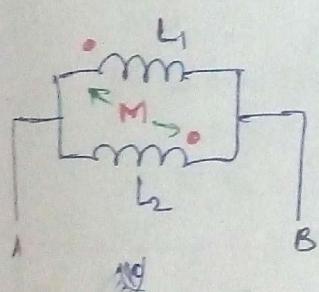
$$-(R_3 + \frac{1}{Cs}) I_1(s) + (R_2 + sL_2 + \frac{1}{Cs} + R_3) I_2(s) = -V_2(s) - MI_1(s)$$



Eq?

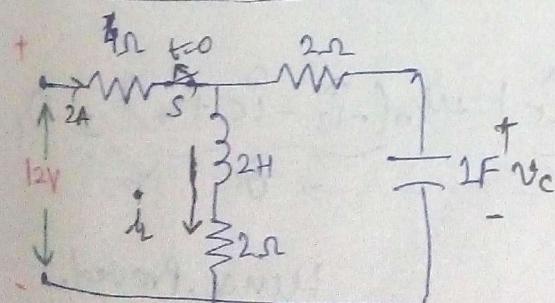

$$i_L(0-) = 2A$$

$$u_L(0-) = 4V$$


at $t=0$, S is opened.

$$i_L(0+) = 2A$$

$$u_L(0+) = 4V$$

$$\frac{di_L}{dt}(0+) = -2A/s$$


$$\frac{du_L}{dt}(0+) = -2A/s$$

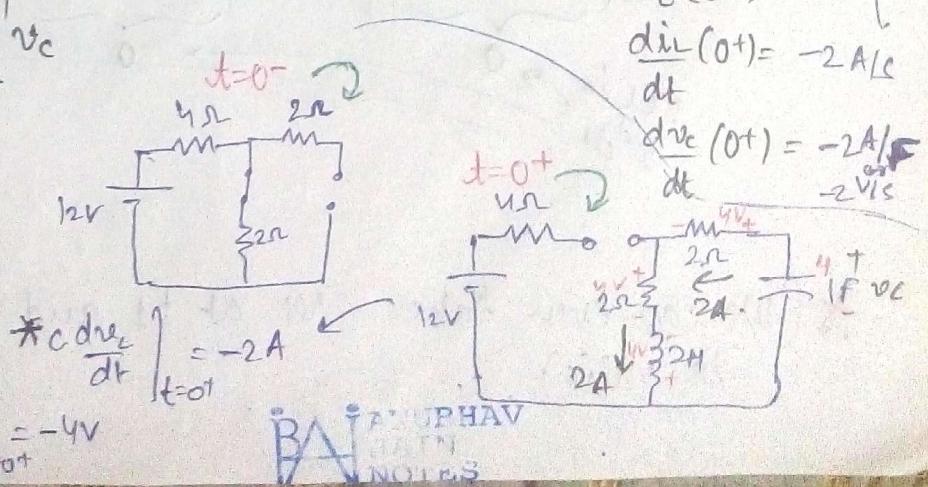


$$* \left. \frac{di_L}{dt} \right|_{t=0+} = -4V$$

TELLEGREN'S TH^m.

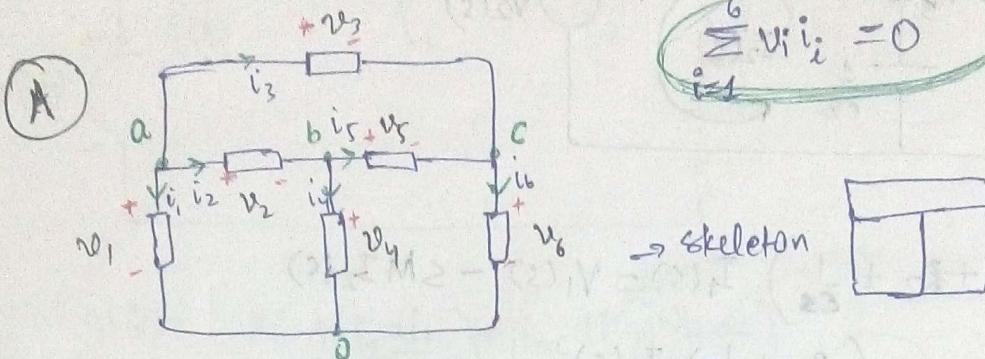Here, all elements are shown absorbing power.




$$\sum_{i=1}^6 V_i i_i = 0$$

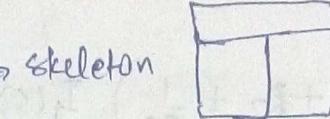

→ Ckt. Topology

Same.

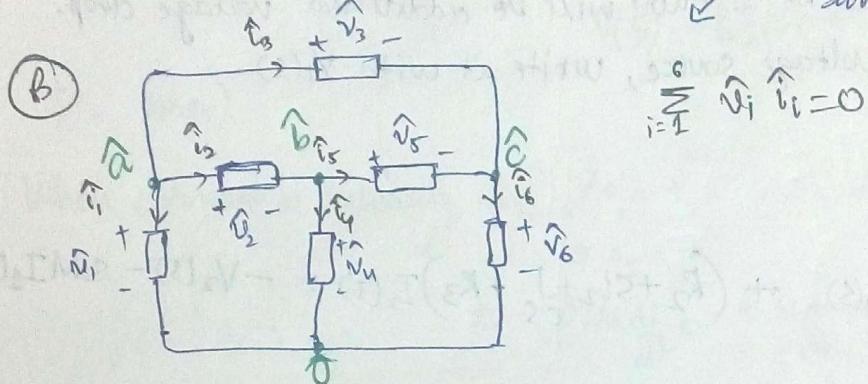

$$\sum_{i=1}^6 \hat{V}_i \hat{i}_i = 0$$

* $V_1 \hat{i}_1 + V_2 \hat{i}_2 + \dots + V_6 \hat{i}_6 = \sum_{i=1}^6 V_i \hat{i}_i = 0$

* $\hat{V}_1 i_1 + \hat{V}_2 i_2 + \dots + \hat{V}_6 i_6 = \sum_{i=1}^6 \hat{V}_i i_i = 0$

Proof of Tellegen's Th^m.

$$\begin{aligned}
 & V_{ao} \hat{i}_1 + V_{ab} \hat{i}_2 + (V_{ao} - V_{bo}) \hat{i}_3 + V_{bo} \hat{i}_4 + (V_{bo} - V_{co}) \hat{i}_5 + V_{co} \hat{i}_6 \\
 & \quad \downarrow \\
 & \quad (V_{ao} - V_{bo}) \\
 & = V_{ao} (\underbrace{\hat{i}_1 + \hat{i}_2 + \hat{i}_3}_0) + V_{bo} (\underbrace{-\hat{i}_2 + \hat{i}_4 + \hat{i}_5}_0) + V_{co} (\underbrace{-\hat{i}_3 - \hat{i}_5 + \hat{i}_6}_0) = 0.
 \end{aligned}$$



KCL in
2nd ckt.

Hence, proved.



(Similar for other part).

* (We can even take V_i at t_1 and \hat{i}_i at t_2 , still Th^m will be valid).

Reciprocity Thm

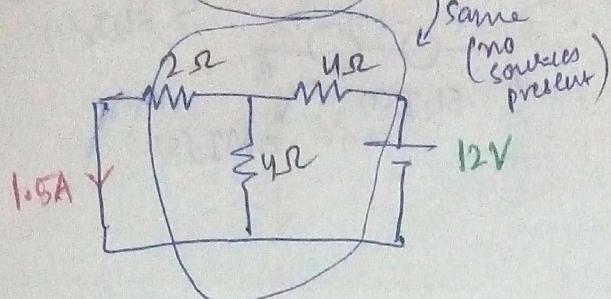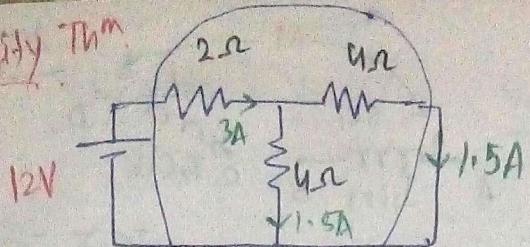

Theory of Reciprocity.

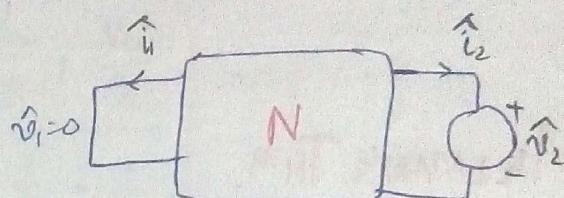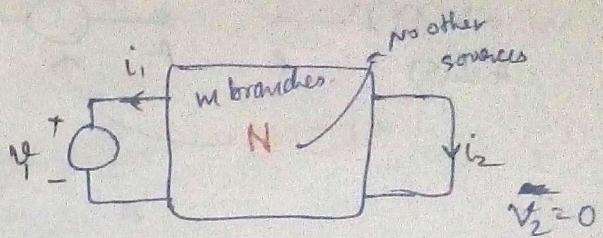

$$v_1 \hat{i}_1 + (0) \hat{i}_2 + \sum_{k=3}^m v_k \hat{i}_k = 0$$

$$(0) \hat{i}_1 + v_2 \hat{i}_2 + \sum_{k=3}^m v_k \hat{i}_k = 0$$

or

$$v_1 \hat{i}_1 + \sum_{k=3}^m R_{kk} \hat{i}_k = v_2 \hat{i}_2 + \sum_{k=3}^m R_{kk} \hat{i}_k = 0$$

$$\Rightarrow v_1 \hat{i}_1 = v_2 \hat{i}_2$$

$$\frac{\hat{i}_2}{v_2} = \frac{\hat{i}_1}{v_1}$$

As in our case,

$$v_1 = v_2 = 12V$$


$$\Rightarrow \hat{i}_2 = \hat{i}_1 = 1.5A$$

Q



Find

$$\mathcal{L}^{-1} \left[\frac{1}{s(s^2+2s+3)} \right]$$

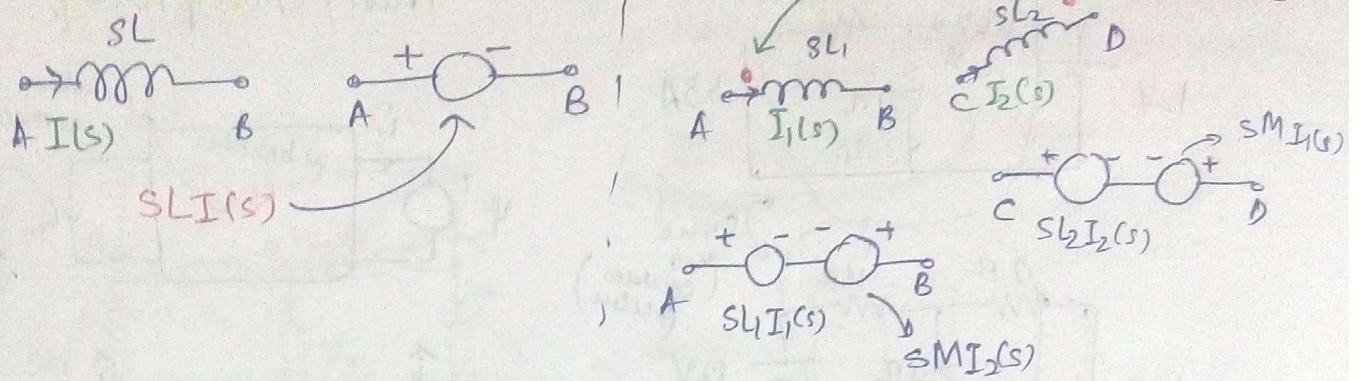
$$\frac{1}{s(s^2+2s+3)} = \frac{1}{s(s+1)^2+2} = ?$$



MILLMAN'S THM.

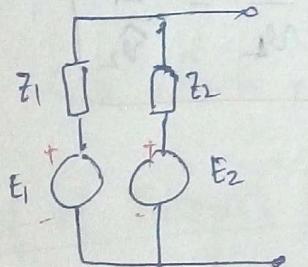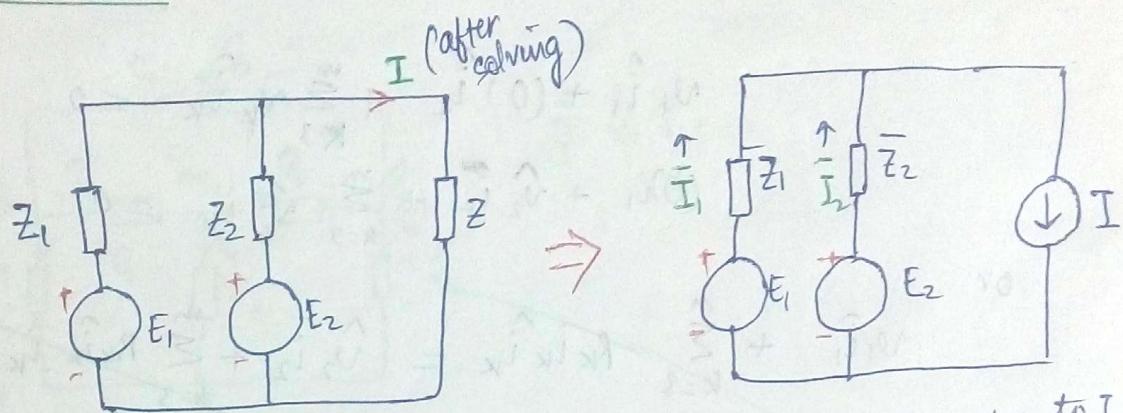

Sup.

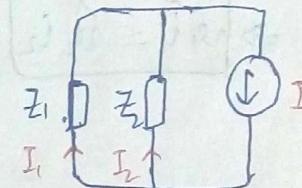


$$I_1 = I \frac{Z_2}{Z_1 + Z_2} \quad \text{due to } I$$

$$I_2 = I \frac{Z_1}{Z_1 + Z_2}$$

$$\frac{E_1 - E_2}{Z_1 + Z_2} + IZ$$

Steady state soln $\Im = j\omega$.

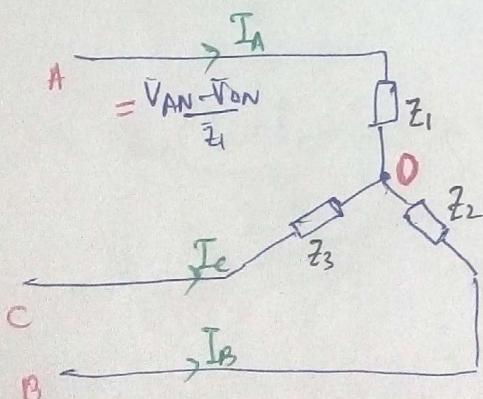

V_{AB} , V_{BC} , V_{CA}	V_{AN} , V_{BN} , V_{CN}
$\bar{I}_A = \frac{\bar{V}_{AO}}{\bar{Z}_1}$	$\bar{I}_B = \frac{\bar{V}_{BO}}{\bar{Z}_2}$
$\bar{I}_C = \frac{\bar{V}_{CO}}{\bar{Z}_3}$	

Apply KCL at O :-

$$\bar{I}_A + \bar{I}_B + \bar{I}_C = 0$$

$$\frac{\bar{V}_{AO}}{\bar{Z}_1} + \frac{\bar{V}_{BO}}{\bar{Z}_2} + \frac{\bar{V}_{CO}}{\bar{Z}_3} = 0$$

$\bar{V} \rightarrow \text{RMS value of } v$

$$\frac{\bar{V}_{AN} - \bar{V}_{ON}}{\bar{Z}_1} + \frac{\bar{V}_{BN} - \bar{V}_{ON}}{\bar{Z}_2} + \frac{\bar{V}_{CN} - \bar{V}_{ON}}{\bar{Z}_3} = 0$$

$$\bar{V}_{ON} \left(\frac{1}{\bar{Z}_1} + \frac{1}{\bar{Z}_2} + \frac{1}{\bar{Z}_3} \right) = \frac{\bar{V}_{AN}}{\bar{Z}_1} + \frac{\bar{V}_{BN}}{\bar{Z}_2} + \frac{\bar{V}_{CN}}{\bar{Z}_3}$$

$$\Rightarrow \bar{V}_{ON} = \frac{\frac{\bar{V}_{AN}}{\bar{Z}_1} + \frac{\bar{V}_{BN}}{\bar{Z}_2} + \frac{\bar{V}_{CN}}{\bar{Z}_3}}{\frac{1}{\bar{Z}_1} + \frac{1}{\bar{Z}_2} + \frac{1}{\bar{Z}_3}}$$

* if $\bar{Z}_1 = \bar{Z}_2 = \bar{Z}_3 \neq 0$

$$\bar{V}_{ON} = 0$$

(as $(\bar{V}_{AN} + \bar{V}_{BN} + \bar{V}_{CN}) = 0$)

* L.T.

$$\mathcal{L}^{-1} \left[\frac{1}{s(s^2+2s+3)} \right]$$

* Method 1

factorise

$$s = \frac{-2 \pm \sqrt{4-12}}{2}$$

$$= -1 \pm j\sqrt{2}$$

a, b

↪ complex.

$$\frac{1}{s(s^2+2s+3)} = \frac{1}{s(s-a)(s-b)} = \frac{A}{s} + \frac{B}{s-a} + \frac{C}{s-b}$$

* Method 2

$$F(s) = \frac{1}{s(s^2+2s+3)} = \frac{A}{s} + G(s)$$

$$\star \text{ (Put } s=0 \text{)} \rightarrow A = \frac{1}{3} \Rightarrow F(s) = \frac{1}{3s} + G(s) = \frac{1}{s(s^2+2s+3)}$$

$$G(s) = \frac{1}{s} \left\{ \frac{1}{s^2+2s+3} - \frac{1}{3} \right\} \Rightarrow G(s) = \frac{(s^2+2s+3)}{3s(s^2+2s+3)} = \frac{-8-2}{3(s^2+2s+3)}$$

$$\Rightarrow F(s) = \frac{1}{3s} - \frac{s+2}{3(s^2+2s+3)}$$

$$= \frac{1}{3s} - \frac{1}{3} \frac{(s+2)}{(s+1)^2+2}$$


$$= \frac{1}{3s} - \frac{1}{3} \left[\frac{(s+1)}{(s+1)^2+2} + \frac{1}{(s+1)^2+2} \right]$$

$$x \quad L \cos \omega t = \frac{s}{s^2 + \omega^2}$$

$$x \quad L e^{-at} \cos \omega t = \frac{sta}{(s+a)^2 + \omega^2}$$

$$x \quad L e^{-at} \sin \omega t = \frac{sw}{(s+a)^2 + \omega^2}$$
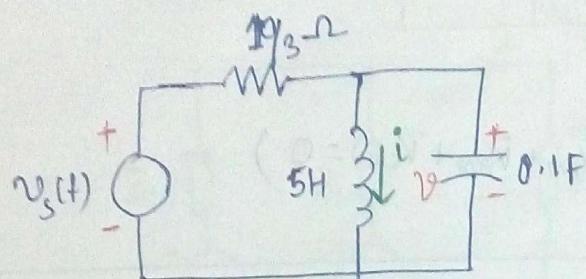
$$\Rightarrow \boxed{\mathcal{L}^{-1}[F(s)] = \frac{1}{3} u(t) - \frac{1}{3} e^{-t} \cos \sqrt{2}t - \frac{1}{3\sqrt{2}} e^{-t} \sin \sqrt{2}t}$$




$$i(0^-) = -1A$$

$$v(0^-) = +5V$$

Calculate $v(t)$ for $t \geq 0$ when
 $v_s(t) = 10 u(t)$

For $t \geq 0$

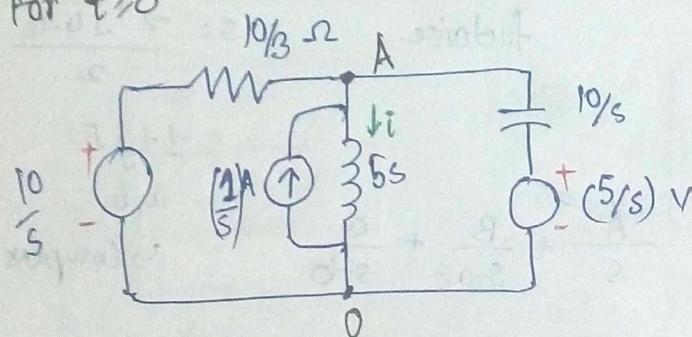

KCL at A :-

$$V_{AO} \left(\frac{3}{10} + \frac{1}{5s} + \frac{8}{10s} \right) \\ = \frac{10/s}{10/3} + \frac{1}{s} + \frac{5/s}{10/s} \\ = \frac{4}{s} + \frac{1}{2}$$

$$V_{AO} \left(\frac{3s + 2 + s^2}{10s} \right) = \frac{8+s}{2s}$$


$$V_{AO} = \frac{5(s+8)}{(s^2+3s+2)} = \frac{5(s+8)}{(s+1)(s+2)} \\ = \frac{A}{s+1} + \frac{B}{s+2}$$

$$A = \frac{5 \times 7}{1} = 35$$

$$B = \frac{5 \times 6}{1} = -30$$

MILLMAN'S THEOREM

24/10/16

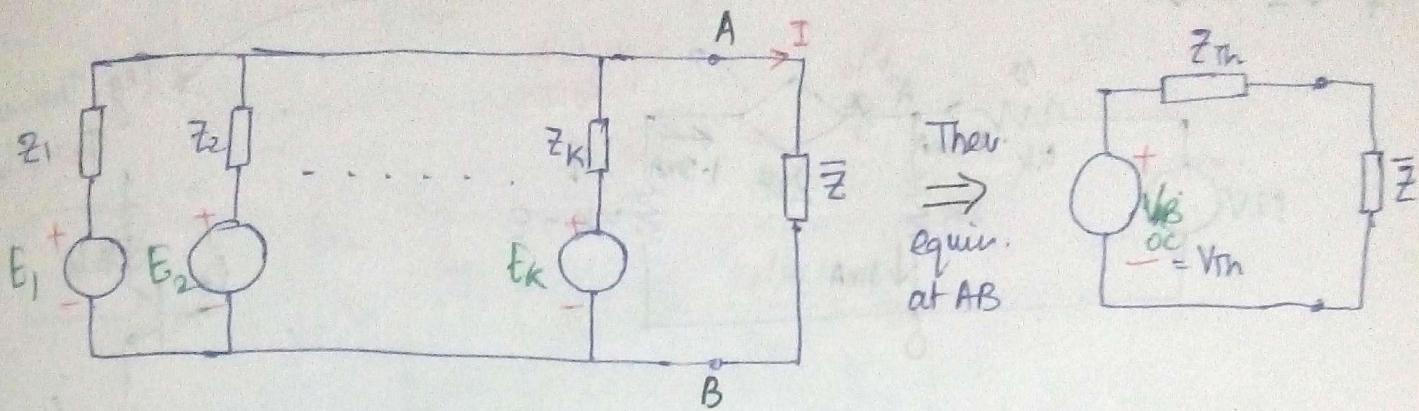

KCL at A with Z removed:-

$$V_{Th} = V_{AB} \text{ (o.c.)}$$



$$\frac{V_{Th}-E_1}{Z_1} + \frac{V_{Th}-E_2}{Z_2} + \dots + \frac{V_{Th}-E_K}{Z_K} = 0$$

$$Y_1(V_{Th}-E_1) + Y_2(V_{Th}-E_2) + \dots + Y_K(V_{Th}-E_K) = 0$$

$$V_{Th} = \frac{E_1 Y_1 + E_2 Y_2 + \dots + E_K Y_K}{Y_1 + Y_2 + Y_3 + \dots + Y_K}$$


$$Z_{Th} = \frac{1}{Y_1 + Y_2 + \dots + Y_K}$$

$$I = \frac{V_{Th}}{Z_{Th} + Z}$$

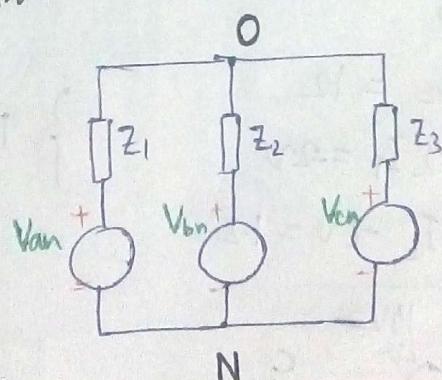
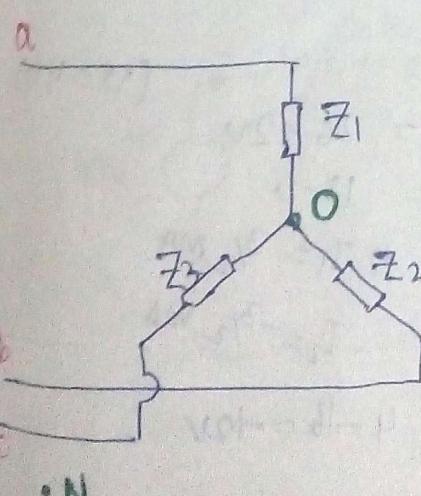


$$V_{ON} = \frac{V_{ao} Y_1 + V_{bo} Y_2 + V_{co} Y_3}{Y_1 + Y_2 + Y_3}$$

$$I_o = \frac{V_{ao} - V_{co}}{Z_1}$$

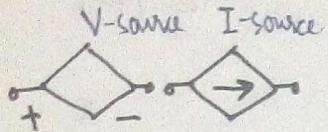

Circuit with dependent sources

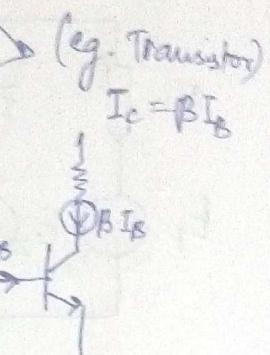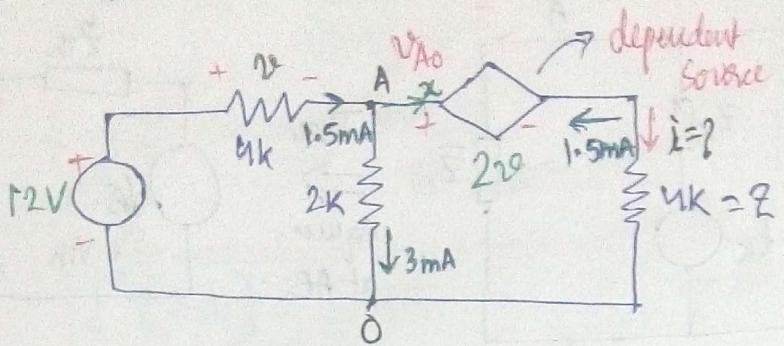

$$\frac{V_{AO} - 12}{4k} + \frac{V_{AO}}{2} + x = 0$$

All currents in mA

$$\frac{V_{AO} - 2x}{4} = 0$$

$$-12 + 2x + V_{AO} = 0$$

$$V = 12 - 2V_{AO}$$


$$\frac{V_{AO}}{4} - 3 + \frac{V_{AO}}{2} + \frac{3V_{AO}}{4} - 6 = 0$$

$$* V_{AO} - 2x \\ = V_{AO} - 24 + 2V_{AO}$$

$$\frac{\beta V_{AO}}{2} = 12$$

$$V_{AO} = 6V$$

$$\Rightarrow V = 12 - 6 = 6V$$

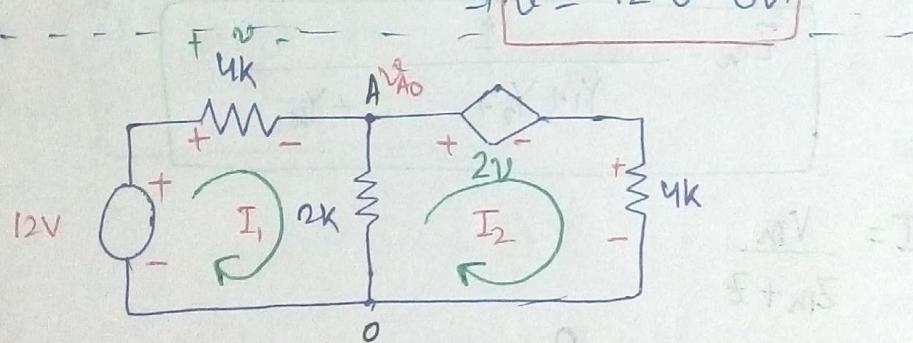

$$6I_1 - 2I_2 = 12$$

$$6I_2 - 2I_1 = -20$$

$$6I_1 + 4I_2 - 20 = 12$$

$$\left. \begin{array}{l} 16I_1 = 36 - 20 \\ 8I_1 = 16 \\ I_1 = 2 \end{array} \right\} (V = 4I_1)$$

$$8I_1 = 16 - 20$$


$$\Rightarrow I_1 = 2mA$$



$$-I_2 = -2mA$$

$$V_{CD} = 4 - 16 = -12V$$

(O.C.)

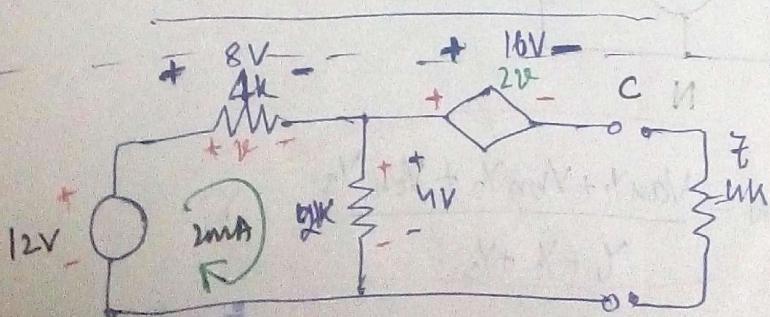While calculating Thévenin's impedance, we deactivate the sources.





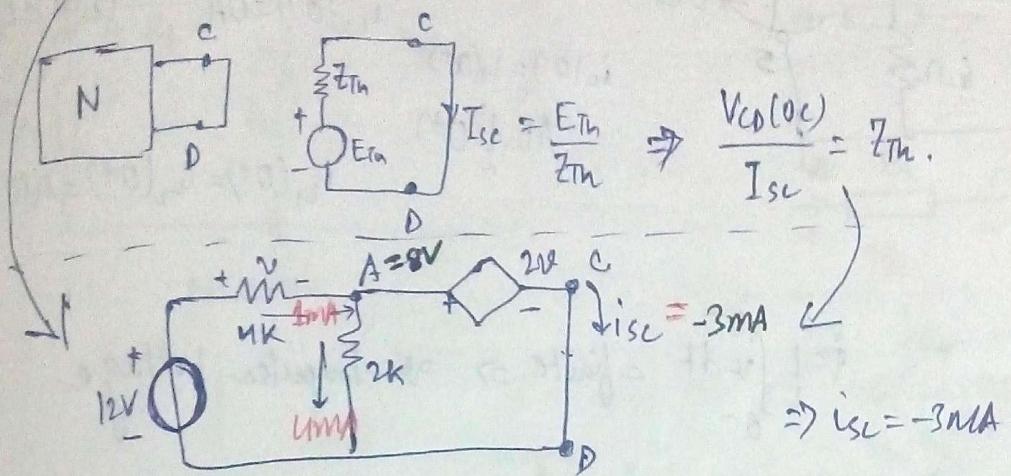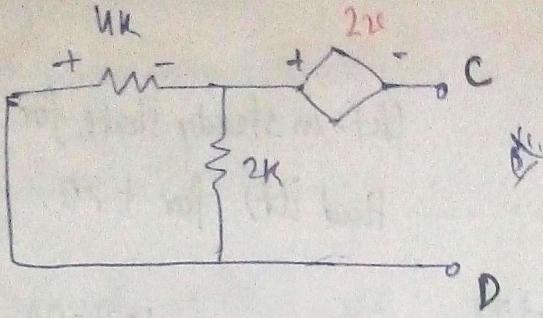

$$NAD = 2k$$


$$\text{Outer loop: } 12 - u - 2k = 0 \Rightarrow u = 4V$$
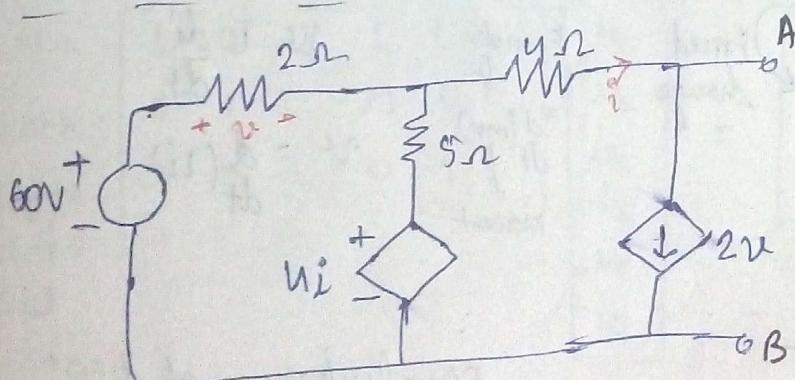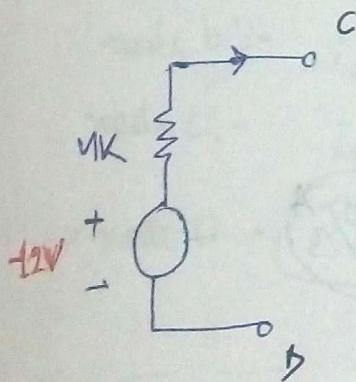
$$\Rightarrow Z_{Th} = \frac{-12}{-6} = 4k$$



Get Thévenin equiv.
between A & B.

26/10/16

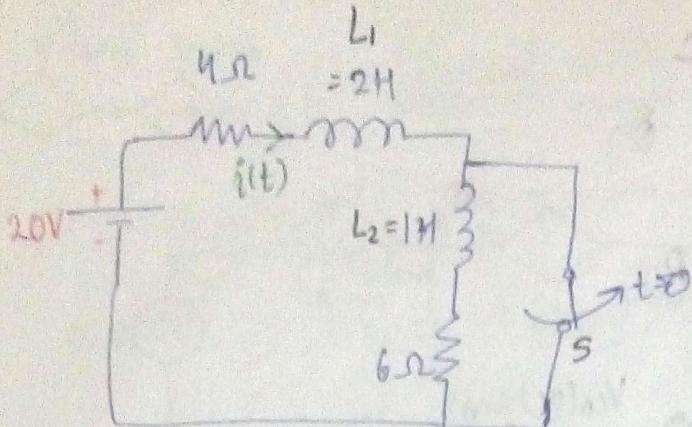Ckt. in steady state for $t < 0$ Find $i(t)$ for $t > 0$.

$$i_{L_2}(0^-) = 0A \quad i_L(0^-) = 5A$$

At $t = 0^+$

$$i_{L_2}(0^+) = i_L(0^+) = i_L(0^+)$$

Let $i(0^+) = x$

$$i = \frac{1}{L} \int_{0^-}^{0^+} v dt = \text{finite} \Rightarrow v = \text{Impulse Voltage}$$

for L_1 :-

$$5 - x = \frac{1}{L_1} \delta(t)$$

for L_2 :-


$$x - 0 = \frac{1}{L_2} \delta(t)$$

$$(5 - x)L_1 = xL_2$$

$$(5 - x)_2 = x \times 1$$

$$\text{or } 3x = 10 \Rightarrow x = 10/3$$

$$x = 10/3$$

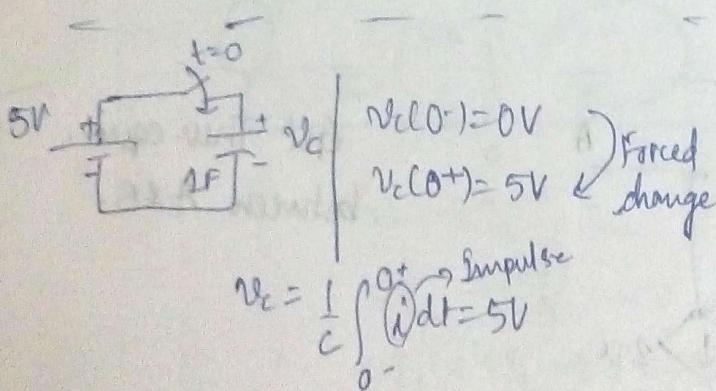

$$\begin{aligned} F &= m dv \\ &= d(mv) \\ &\downarrow \text{moment} \end{aligned}$$

$$\begin{aligned} v &= L \frac{di}{dt} \\ v &= \frac{d}{dt} (Li) \end{aligned}$$

$$L = \frac{\Phi}{\frac{d\Phi}{dt}}$$

$$Li = \Phi$$

Flux linkage at $t = 0^-$

$$2 \times 5 + 1 \times 0 = 10$$

$$10 = 3x \Rightarrow x = \frac{10}{3} A$$

Flux linkage at $t = 0^+$

$$2 \times 2 + 1 \times 2 = 3x$$

Flux linkage through
it cannot change
instantly \Rightarrow More fundamental